

# 25

# CAPACITANCE

## 25-1 WHAT IS PHYSICS?

One goal of physics is to provide the basic science for practical devices designed by engineers. The focus of this chapter is on one extremely common example—the capacitor, a device in which electrical energy can be stored. For example, the batteries in a camera store energy in the photoflash unit by charging a capacitor. The batteries can supply energy at only a modest rate, too slowly for the photoflash unit to emit a flash of light. However, once the capacitor is charged, it can supply energy at a much greater rate when the photoflash unit is triggered—enough energy to allow the unit to emit a burst of bright light.

The physics of capacitors can be generalized to other devices and to any situation involving electric fields. For example, Earth's atmospheric electric field is modeled by meteorologists as being produced by a huge spherical capacitor that partially discharges via lightning. The charge that skiers collect as they slide along snow can be modeled as being stored in a capacitor that frequently discharges as sparks (which can be seen by nighttime skiers on dry snow).


The first step in our discussion of capacitors is to determine how much charge can be stored. This “how much” is called capacitance.

## 25-2 Capacitance


Figure 25-1 shows some of the many sizes and shapes of capacitors. Figure 25-2 shows the basic elements of *any* capacitor—two isolated conductors of any



**Fig. 25-1** An assortment of capacitors.

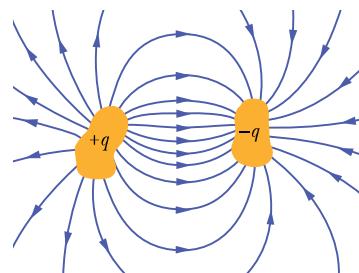

**Fig. 25-2** Two conductors, isolated electrically from each other and from their surroundings, form a *capacitor*. When the capacitor is charged, the charges on the conductors, or *plates* as they are called, have the same magnitude  $q$  but opposite signs.  
(Paul Silvermann/Fundamental Photographs)

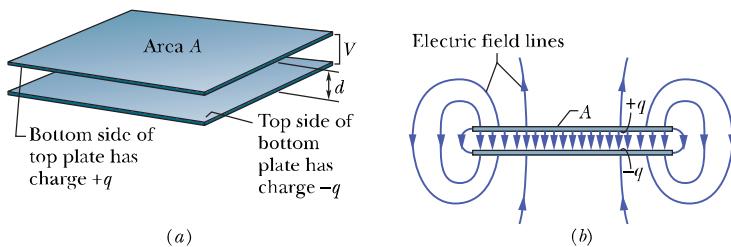

**Fig. 25-3** (a) A parallel-plate capacitor, made up of two plates of area  $A$  separated by a distance  $d$ . The charges on the facing plate surfaces have the same magnitude  $q$  but opposite signs. (b) As the field lines show, the electric field due to the charged plates is uniform in the central region between the plates. The field is not uniform at the edges of the plates, as indicated by the “fringing” of the field lines there.

shape. No matter what their geometry, flat or not, we call these conductors *plates*.

Figure 25-3a shows a less general but more conventional arrangement, called a *parallel-plate capacitor*, consisting of two parallel conducting plates of area  $A$  separated by a distance  $d$ . The symbol we use to represent a capacitor ( $\text{+}\text{-}$ ) is based on the structure of a parallel-plate capacitor but is used for capacitors of all geometries. We assume for the time being that no material medium (such as glass or plastic) is present in the region between the plates. In Section 25-6, we shall remove this restriction.

When a capacitor is *charged*, its plates have charges of equal magnitudes but opposite signs:  $+q$  and  $-q$ . However, we refer to the *charge of a capacitor* as being  $q$ , the absolute value of these charges on the plates. (Note that  $q$  is not the net charge on the capacitor, which is zero.)

Because the plates are conductors, they are equipotential surfaces; all points on a plate are at the same electric potential. Moreover, there is a potential difference between the two plates. For historical reasons, we represent the absolute value of this potential difference with  $V$  rather than with the  $\Delta V$  we used in previous notation.

The charge  $q$  and the potential difference  $V$  for a capacitor are proportional to each other; that is,

$$q = CV. \quad (25-1)$$

The proportionality constant  $C$  is called the **capacitance** of the capacitor. Its value depends only on the geometry of the plates and *not* on their charge or potential difference. The capacitance is a measure of how much charge must be put on the plates to produce a certain potential difference between them: The *greater the capacitance, the more charge is required*.


The SI unit of capacitance that follows from Eq. 25-1 is the coulomb per volt. This unit occurs so often that it is given a special name, the **farad** (F):

$$1 \text{ farad} = 1 \text{ F} = 1 \text{ coulomb per volt} = 1 \text{ C/V}. \quad (25-2)$$

As you will see, the farad is a very large unit. Submultiples of the farad, such as the microfarad ( $1 \mu\text{F} = 10^{-6} \text{ F}$ ) and the picofarad ( $1 \text{ pF} = 10^{-12} \text{ F}$ ), are more convenient units in practice.

## Charging a Capacitor

One way to charge a capacitor is to place it in an electric circuit with a battery. An *electric circuit* is a path through which charge can flow. A *battery* is a device

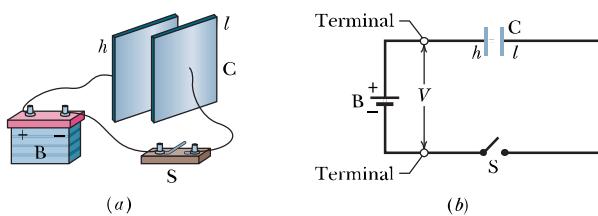

**Fig. 25-4** (a) Battery B, switch S, and plates h and l of capacitor C, connected in a circuit. (b) A schematic diagram with the *circuit elements* represented by their symbols.

that maintains a certain potential difference between its *terminals* (points at which charge can enter or leave the battery) by means of internal electrochemical reactions in which electric forces can move internal charge.

In Fig. 25-4a, a battery B, a switch S, an uncharged capacitor C, and interconnecting wires form a circuit. The same circuit is shown in the *schematic diagram* of Fig. 25-4b, in which the symbols for a battery, a switch, and a capacitor represent those devices. The battery maintains potential difference  $V$  between its terminals. The terminal of higher potential is labeled + and is often called the *positive terminal*; the terminal of lower potential is labeled - and is often called the *negative terminal*.

The circuit shown in Figs. 25-4a and b is said to be *incomplete* because switch S is *open*; that is, the switch does not electrically connect the wires attached to it. When the switch is *closed*, electrically connecting those wires, the circuit is complete and charge can then flow through the switch and the wires. As we discussed in Chapter 21, the charge that can flow through a conductor, such as a wire, is that of electrons. When the circuit of Fig. 25-4 is completed, electrons are driven through the wires by an electric field that the battery sets up in the wires. The field drives electrons from capacitor plate h to the positive terminal of the battery; thus, plate h, losing electrons, becomes positively charged. The field drives just as many electrons from the negative terminal of the battery to capacitor plate l; thus, plate l, gaining electrons, becomes negatively charged *just as much* as plate h, losing electrons, becomes positively charged.

Initially, when the plates are uncharged, the potential difference between them is zero. As the plates become oppositely charged, that potential difference increases until it equals the potential difference  $V$  between the terminals of the battery. Then plate h and the positive terminal of the battery are at the same potential, and there is no longer an electric field in the wire between them. Similarly, plate l and the negative terminal reach the same potential, and there is then no electric field in the wire between them. Thus, with the field zero, there is no further drive of electrons. The capacitor is then said to be *fully charged*, with a potential difference  $V$  and charge  $q$  that are related by Eq. 25-1.

In this book we assume that during the charging of a capacitor and afterward, charge cannot pass from one plate to the other across the gap separating them. Also, we assume that a capacitor can retain (or *store*) charge indefinitely, until it is put into a circuit where it can be *discharged*.



### CHECKPOINT 1

Does the capacitance  $C$  of a capacitor increase, decrease, or remain the same (a) when the charge  $q$  on it is doubled and (b) when the potential difference  $V$  across it is tripled?

## 25-3 Calculating the Capacitance

Our goal here is to calculate the capacitance of a capacitor once we know its geometry. Because we shall consider a number of different geometries, it seems wise to develop a general plan to simplify the work. In brief our plan is as follows: (1) Assume a charge  $q$  on the plates; (2) calculate the electric field  $\vec{E}$  between the plates in terms of this charge, using Gauss' law; (3) knowing  $\vec{E}$ , calculate the potential difference  $V$  between the plates from Eq. 24-18; (4) calculate  $C$  from Eq. 25-1.

Before we start, we can simplify the calculation of both the electric field and the potential difference by making certain assumptions. We discuss each in turn.

### Calculating the Electric Field

To relate the electric field  $\vec{E}$  between the plates of a capacitor to the charge  $q$  on either plate, we shall use Gauss' law:

$$\epsilon_0 \oint \vec{E} \cdot d\vec{A} = q. \quad (25-3)$$

Here  $q$  is the charge enclosed by a Gaussian surface and  $\oint \vec{E} \cdot d\vec{A}$  is the net electric flux through that surface. In all cases that we shall consider, the Gaussian surface will be such that whenever there is an electric flux through it,  $\vec{E}$  will have a uniform magnitude  $E$  and the vectors  $\vec{E}$  and  $d\vec{A}$  will be parallel. Equation 25-3 then reduces to

$$q = \epsilon_0 E A \quad (\text{special case of Eq. 25-3}), \quad (25-4)$$

in which  $A$  is the area of that part of the Gaussian surface through which there is a flux. For convenience, we shall always draw the Gaussian surface in such a way that it completely encloses the charge on the positive plate; see Fig. 25-5 for an example.

### Calculating the Potential Difference

In the notation of Chapter 24 (Eq. 24-18), the potential difference between the plates of a capacitor is related to the field  $\vec{E}$  by

$$V_f - V_i = - \int_i^f \vec{E} \cdot d\vec{s}, \quad (25-5)$$

in which the integral is to be evaluated along any path that starts on one plate and ends on the other. We shall always choose a path that follows an electric field line, from the negative plate to the positive plate. For this path, the vectors  $\vec{E}$  and  $d\vec{s}$  will have opposite directions; so the dot product  $\vec{E} \cdot d\vec{s}$  will be equal to  $-E ds$ . Thus, the right side of Eq. 25-5 will then be positive. Letting  $V$  represent the difference  $V_f - V_i$ , we can then recast Eq. 25-5 as

$$V = \int_{-}^{+} E ds \quad (\text{special case of Eq. 25-5}), \quad (25-6)$$


in which the  $-$  and  $+$  remind us that our path of integration starts on the negative plate and ends on the positive plate.

We are now ready to apply Eqs. 25-4 and 25-6 to some particular cases.


### A Parallel-Plate Capacitor

We assume, as Fig. 25-5 suggests, that the plates of our parallel-plate capacitor are so large and so close together that we can neglect the fringing of the electric field

We use Gauss' law to relate  $q$  and  $E$ . Then we integrate the  $E$  to get the potential difference.

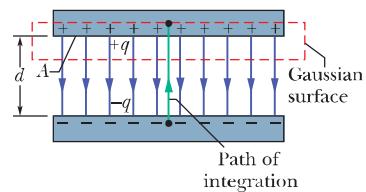

**Fig. 25-5** A charged parallel-plate capacitor. A Gaussian surface encloses the charge on the positive plate. The integration of Eq. 25-6 is taken along a path extending directly from the negative plate to the positive plate.

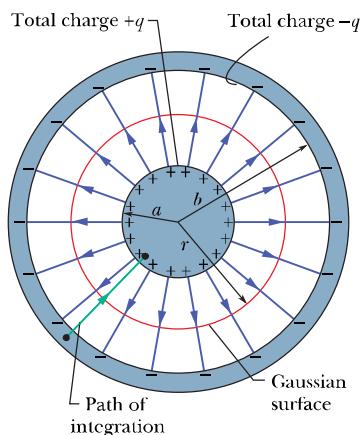

**Fig. 25-6** A cross section of a long cylindrical capacitor, showing a cylindrical Gaussian surface of radius  $r$  (that encloses the positive plate) and the radial path of integration along which Eq. 25-6 is to be applied. This figure also serves to illustrate a spherical capacitor in a cross section through its center.

at the edges of the plates, taking  $\vec{E}$  to be constant throughout the region between the plates.

We draw a Gaussian surface that encloses just the charge  $q$  on the positive plate, as in Fig. 25-5. From Eq. 25-4 we can then write

$$q = \epsilon_0 E A, \quad (25-7)$$

where  $A$  is the area of the plate.

Equation 25-6 yields

$$V = \int_{-}^{+} E ds = E \int_0^d ds = Ed. \quad (25-8)$$

In Eq. 25-8,  $E$  can be placed outside the integral because it is a constant; the second integral then is simply the plate separation  $d$ .

If we now substitute  $q$  from Eq. 25-7 and  $V$  from Eq. 25-8 into the relation  $q = CV$  (Eq. 25-1), we find

$$C = \frac{\epsilon_0 A}{d} \quad (\text{parallel-plate capacitor}). \quad (25-9)$$

Thus, the capacitance does indeed depend only on geometrical factors—namely, the plate area  $A$  and the plate separation  $d$ . Note that  $C$  increases as we increase area  $A$  or decrease separation  $d$ .

As an aside, we point out that Eq. 25-9 suggests one of our reasons for writing the electrostatic constant in Coulomb's law in the form  $1/4\pi\epsilon_0$ . If we had not done so, Eq. 25-9—which is used more often in engineering practice than Coulomb's law—would have been less simple in form. We note further that Eq. 25-9 permits us to express the permittivity constant  $\epsilon_0$  in a unit more appropriate for use in problems involving capacitors; namely,

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m} = 8.85 \text{ pF/m}. \quad (25-10)$$

We have previously expressed this constant as

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2. \quad (25-11)$$

### A Cylindrical Capacitor

Figure 25-6 shows, in cross section, a cylindrical capacitor of length  $L$  formed by two coaxial cylinders of radii  $a$  and  $b$ . We assume that  $L \gg b$  so that we can neglect the fringing of the electric field that occurs at the ends of the cylinders. Each plate contains a charge of magnitude  $q$ .

As a Gaussian surface, we choose a cylinder of length  $L$  and radius  $r$ , closed by end caps and placed as is shown in Fig. 25-6. It is coaxial with the cylinders and encloses the central cylinder and thus also the charge  $q$  on that cylinder. Equation 25-4 then relates that charge and the field magnitude  $E$  as

$$q = \epsilon_0 E A = \epsilon_0 E (2\pi r L),$$

in which  $2\pi r L$  is the area of the curved part of the Gaussian surface. There is no flux through the end caps. Solving for  $E$  yields

$$E = \frac{q}{2\pi\epsilon_0 L r}. \quad (25-12)$$

Substitution of this result into Eq. 25-6 yields

$$V = \int_{-}^{+} E ds = -\frac{q}{2\pi\epsilon_0 L} \int_b^a \frac{dr}{r} = \frac{q}{2\pi\epsilon_0 L} \ln\left(\frac{b}{a}\right), \quad (25-13)$$

where we have used the fact that here  $ds = -dr$  (we integrated radially inward). From the relation  $C = q/V$ , we then have

$$C = 2\pi\epsilon_0 \frac{L}{\ln(b/a)} \quad (\text{cylindrical capacitor}). \quad (25-14)$$

We see that the capacitance of a cylindrical capacitor, like that of a parallel-plate capacitor, depends only on geometrical factors, in this case the length  $L$  and the two radii  $b$  and  $a$ .

### A Spherical Capacitor

Figure 25-6 can also serve as a central cross section of a capacitor that consists of two concentric spherical shells, of radii  $a$  and  $b$ . As a Gaussian surface we draw a sphere of radius  $r$  concentric with the two shells; then Eq. 25-4 yields

$$q = \epsilon_0 E A = \epsilon_0 E (4\pi r^2),$$

in which  $4\pi r^2$  is the area of the spherical Gaussian surface. We solve this equation for  $E$ , obtaining

$$E = \frac{1}{4\pi\epsilon_0} \frac{q}{r^2}, \quad (25-15)$$

which we recognize as the expression for the electric field due to a uniform spherical charge distribution (Eq. 23-15).

If we substitute this expression into Eq. 25-6, we find

$$V = \int_{-\infty}^{+\infty} E ds = -\frac{q}{4\pi\epsilon_0} \int_b^a \frac{dr}{r^2} = \frac{q}{4\pi\epsilon_0} \left( \frac{1}{a} - \frac{1}{b} \right) = \frac{q}{4\pi\epsilon_0} \frac{b-a}{ab}, \quad (25-16)$$

where again we have substituted  $-dr$  for  $ds$ . If we now substitute Eq. 25-16 into Eq. 25-1 and solve for  $C$ , we find

$$C = 4\pi\epsilon_0 \frac{ab}{b-a} \quad (\text{spherical capacitor}). \quad (25-17)$$

### An Isolated Sphere

We can assign a capacitance to a *single* isolated spherical conductor of radius  $R$  by assuming that the “missing plate” is a conducting sphere of infinite radius. After all, the field lines that leave the surface of a positively charged isolated conductor must end somewhere; the walls of the room in which the conductor is housed can serve effectively as our sphere of infinite radius.

To find the capacitance of the conductor, we first rewrite Eq. 25-17 as

$$C = 4\pi\epsilon_0 \frac{a}{1 - a/b}.$$

If we then let  $b \rightarrow \infty$  and substitute  $R$  for  $a$ , we find

$$C = 4\pi\epsilon_0 R \quad (\text{isolated sphere}). \quad (25-18)$$

Note that this formula and the others we have derived for capacitance (Eqs. 25-9, 25-14, and 25-17) involve the constant  $\epsilon_0$  multiplied by a quantity that has the dimensions of a length.

#### CHECKPOINT 2

For capacitors charged by the same battery, does the charge stored by the capacitor increase, decrease, or remain the same in each of the following situations? (a) The plate separation of a parallel-plate capacitor is increased. (b) The radius of the inner cylinder of a cylindrical capacitor is increased. (c) The radius of the outer spherical shell of a spherical capacitor is increased.


**Sample Problem****Charging the plates in a parallel-plate capacitor**

In Fig. 25-7a, switch S is closed to connect the uncharged capacitor of capacitance  $C = 0.25 \mu\text{F}$  to the battery of potential difference  $V = 12 \text{ V}$ . The lower capacitor plate has thickness  $L = 0.50 \text{ cm}$  and face area  $A = 2.0 \times 10^{-4} \text{ m}^2$ , and it consists of copper, in which the density of conduction electrons is  $n = 8.49 \times 10^{28} \text{ electrons/m}^3$ . From what depth  $d$  within the plate (Fig. 25-7b) must electrons move to the plate face as the capacitor becomes charged?

**KEY IDEA**

The charge collected on the plate is related to the capacitance and the potential difference across the capacitor by Eq. 25-1 ( $q = CV$ ).

**Calculations:** Because the lower plate is connected to the negative terminal of the battery, conduction electrons move up to the face of the plate. From Eq. 25-1, the total charge

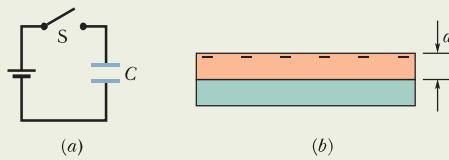

**Fig. 25-7** (a) A battery and capacitor circuit. (b) The lower capacitor plate.

magnitude that collects there is

$$\begin{aligned} q &= CV = (0.25 \times 10^{-6} \text{ F})(12 \text{ V}) \\ &= 3.0 \times 10^{-6} \text{ C}. \end{aligned}$$

Dividing this result by  $e$  gives us the number  $N$  of conduction electrons that come up to the face:

$$\begin{aligned} N &= \frac{q}{e} = \frac{3.0 \times 10^{-6} \text{ C}}{1.602 \times 10^{-19} \text{ C}} \\ &= 1.873 \times 10^{13} \text{ electrons}. \end{aligned}$$

These electrons come from a volume that is the product of the face area  $A$  and the depth  $d$  we seek. Thus, from the density of conduction electrons (number per volume), we can write

$$n = \frac{N}{Ad},$$

or

$$\begin{aligned} d &= \frac{N}{An} = \frac{1.873 \times 10^{13} \text{ electrons}}{(2.0 \times 10^{-4} \text{ m}^2)(8.49 \times 10^{28} \text{ electrons/m}^3)} \\ &= 1.1 \times 10^{-12} \text{ m} = 1.1 \text{ pm}. \quad (\text{Answer}) \end{aligned}$$

In common speech, we would say that the battery charges the capacitor by supplying the charged particles. But what the battery really does is set up an electric field in the wires and plate such that electrons very close to the plate face move up to the negative face.



Additional examples, video, and practice available at WileyPLUS

**25-4 Capacitors in Parallel and in Series**

When there is a combination of capacitors in a circuit, we can sometimes replace that combination with an **equivalent capacitor**—that is, a single capacitor that has the same capacitance as the actual combination of capacitors. With such a replacement, we can simplify the circuit, affording easier solutions for unknown quantities of the circuit. Here we discuss two basic combinations of capacitors that allow such a replacement.

**Capacitors in Parallel**

Figure 25-8a shows an electric circuit in which three capacitors are connected *in parallel* to battery B. This description has little to do with how the capacitor plates are drawn. Rather, “in parallel” means that the capacitors are directly wired together at one plate and directly wired together at the other plate, and that the same potential difference  $V$  is applied across the two groups of wired-together plates. Thus, each capacitor has the same potential difference  $V$ , which produces charge on the capacitor. (In Fig. 25-8a, the applied potential  $V$  is maintained by the battery.) In general,

## 25-4 CAPACITORS IN PARALLEL AND IN SERIES

663



When a potential difference  $V$  is applied across several capacitors connected in parallel, that potential difference  $V$  is applied across each capacitor. The total charge  $q$  stored on the capacitors is the sum of the charges stored on all the capacitors.

When we analyze a circuit of capacitors in parallel, we can simplify it with this mental replacement:



Capacitors connected in parallel can be replaced with an equivalent capacitor that has the same *total* charge  $q$  and the same potential difference  $V$  as the actual capacitors.

(You might remember this result with the nonsense word “par-V,” which is close to “party,” to mean “capacitors in parallel have the same  $V$ .”) Figure 25-8b shows the equivalent capacitor (with equivalent capacitance  $C_{eq}$ ) that has replaced the three capacitors (with actual capacitances  $C_1$ ,  $C_2$ , and  $C_3$ ) of Fig. 25-8a.

To derive an expression for  $C_{eq}$  in Fig. 25-8b, we first use Eq. 25-1 to find the charge on each actual capacitor:

$$q_1 = C_1 V, \quad q_2 = C_2 V, \quad \text{and} \quad q_3 = C_3 V.$$

The total charge on the parallel combination of Fig. 25-8a is then

$$q = q_1 + q_2 + q_3 = (C_1 + C_2 + C_3)V.$$

The equivalent capacitance, with the same total charge  $q$  and applied potential difference  $V$  as the combination, is then

$$C_{eq} = \frac{q}{V} = C_1 + C_2 + C_3,$$

a result that we can easily extend to any number  $n$  of capacitors, as

$$C_{eq} = \sum_{j=1}^n C_j \quad (\text{n capacitors in parallel}). \quad (25-19)$$

Thus, to find the equivalent capacitance of a parallel combination, we simply add the individual capacitances.


### Capacitors in Series

Figure 25-9a shows three capacitors connected *in series* to battery B. This description has little to do with how the capacitors are drawn. Rather, “in series” means that the capacitors are wired serially, one after the other, and that a potential difference  $V$  is applied across the two ends of the series. (In Fig. 25-9a, this potential difference  $V$  is maintained by battery B.) The potential differences that then exist across the capacitors in the series produce identical charges  $q$  on them.




When a potential difference  $V$  is applied across several capacitors connected in series, the capacitors have identical charge  $q$ . The sum of the potential differences across all the capacitors is equal to the applied potential difference  $V$ .

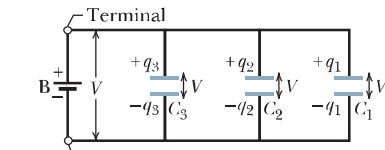We can explain how the capacitors end up with identical charge by following a *chain reaction* of events, in which the charging of each capacitor causes the charging of the next capacitor. We start with capacitor 3 and work upward to capacitor 1. When the battery is first connected to the series of capacitors, it




(a)

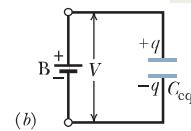Parallel capacitors and their equivalent have the same  $V$  (“par-V”).



(b)

**Fig. 25-8** (a) Three capacitors connected in parallel to battery B. The battery maintains potential difference  $V$  across its terminals and thus across *each* capacitor. (b) The equivalent capacitor, with capacitance  $C_{eq}$ , replaces the parallel combination.

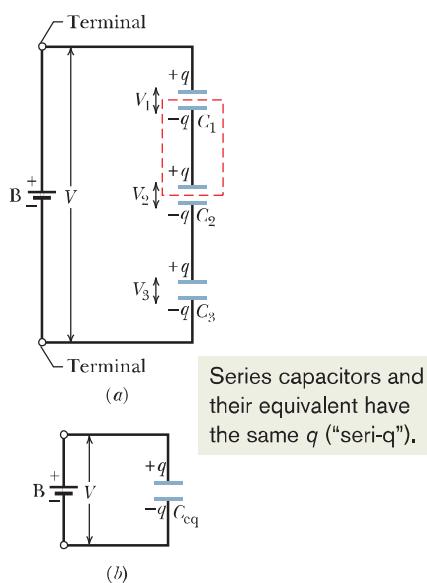

**Fig. 25-9** (a) Three capacitors connected in series to battery B. The battery maintains potential difference  $V$  between the top and bottom plates of the series combination. (b) The equivalent capacitor, with capacitance  $C_{eq}$ , replaces the series combination.

produces charge  $-q$  on the bottom plate of capacitor 3. That charge then repels negative charge from the top plate of capacitor 3 (leaving it with charge  $+q$ ). The repelled negative charge moves to the bottom plate of capacitor 2 (giving it charge  $-q$ ). That charge on the bottom plate of capacitor 2 then repels negative charge from the top plate of capacitor 2 (leaving it with charge  $+q$ ) to the bottom plate of capacitor 1 (giving it charge  $-q$ ). Finally, the charge on the bottom plate of capacitor 1 helps move negative charge from the top plate of capacitor 1 to the battery, leaving that top plate with charge  $+q$ .

Here are two important points about capacitors in series:

- When charge is shifted from one capacitor to another in a series of capacitors, it can move along only one route, such as from capacitor 3 to capacitor 2 in Fig. 25-9a. If there are additional routes, the capacitors are not in series.
- The battery directly produces charges on only the two plates to which it is connected (the bottom plate of capacitor 3 and the top plate of capacitor 1 in Fig. 25-9a). Charges that are produced on the other plates are due merely to the shifting of charge already there. For example, in Fig. 25-9a, the part of the circuit enclosed by dashed lines is electrically isolated from the rest of the circuit. Thus, the net charge of that part cannot be changed by the battery—its charge can only be redistributed.

When we analyze a circuit of capacitors in series, we can simplify it with this mental replacement:



Capacitors that are connected in series can be replaced with an equivalent capacitor that has the same charge  $q$  and the same *total* potential difference  $V$  as the actual series capacitors.

(You might remember this with the nonsense word “seri-q” to mean “capacitors in series have the same  $q$ .”) Figure 25-9b shows the equivalent capacitor (with equivalent capacitance  $C_{eq}$ ) that has replaced the three actual capacitors (with actual capacitances  $C_1$ ,  $C_2$ , and  $C_3$ ) of Fig. 25-9a.

To derive an expression for  $C_{eq}$  in Fig. 25-9b, we first use Eq. 25-1 to find the potential difference of each actual capacitor:

$$V_1 = \frac{q}{C_1}, \quad V_2 = \frac{q}{C_2}, \quad \text{and} \quad V_3 = \frac{q}{C_3}.$$

The total potential difference  $V$  due to the battery is the sum of these three potential differences. Thus,

$$V = V_1 + V_2 + V_3 = q \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right).$$

The equivalent capacitance is then

$$C_{eq} = \frac{q}{V} = \frac{1}{1/C_1 + 1/C_2 + 1/C_3},$$

or

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}.$$

We can easily extend this to any number  $n$  of capacitors as

$$\frac{1}{C_{eq}} = \sum_{j=1}^n \frac{1}{C_j} \quad (\text{n capacitors in series}). \quad (25-20)$$

Using Eq. 25-20 you can show that the equivalent capacitance of a series of capacitances is always *less* than the least capacitance in the series.



### CHECKPOINT 3

A battery of potential  $V$  stores charge  $q$  on a combination of two identical capacitors. What are the potential difference across and the charge on either capacitor if the capacitors are (a) in parallel and (b) in series?

## 25-4 CAPACITORS IN PARALLEL AND IN SERIES

## Sample Problem

## Capacitors in parallel and in series

(a) Find the equivalent capacitance for the combination of capacitances shown in Fig. 25-10a, across which potential difference  $V$  is applied. Assume

$$C_1 = 12.0 \mu\text{F}, \quad C_2 = 5.30 \mu\text{F}, \quad \text{and} \quad C_3 = 4.50 \mu\text{F}$$

## KEY IDEA

Any capacitors connected in series can be replaced with their equivalent capacitor, and any capacitors connected in parallel can be replaced with their equivalent capacitor. Therefore, we should first check whether any of the capacitors in Fig. 25-10a are in parallel or series.

**Finding equivalent capacitance:** Capacitors 1 and 3 are connected one after the other, but are they in series? No. The potential  $V$  that is applied to the capacitors produces charge on the bottom plate of capacitor 3. That charge causes charge to shift from the top plate of capacitor 3. However, note that the shifting charge can move to the bottom plates of both capacitor 1 and capacitor 2. Because there is more than one route for the shifting


charge, capacitor 3 is not in series with capacitor 1 (or capacitor 2).

Are capacitor 1 and capacitor 2 in parallel? Yes. Their top plates are directly wired together and their bottom plates are directly wired together, and electric potential is applied between the top-plate pair and the bottom-plate pair. Thus, capacitor 1 and capacitor 2 are in parallel, and Eq. 25-19 tells us that their equivalent capacitance  $C_{12}$  is

$$C_{12} = C_1 + C_2 = 12.0 \mu\text{F} + 5.30 \mu\text{F} = 17.3 \mu\text{F}$$

In Fig. 25-10b, we have replaced capacitors 1 and 2 with their equivalent capacitor, called capacitor 12 (say “one two” and not “twelve”). (The connections at points A and B are exactly the same in Figs. 25-10a and b.)

Is capacitor 12 in series with capacitor 3? Again applying the test for series capacitances, we see that the charge that shifts from the top plate of capacitor 3 must entirely go to the bottom plate of capacitor 12. Thus, capacitor 12 and capacitor 3 are in series, and we can replace them with their equivalent  $C_{123}$  (“one two three”), as shown in Fig. 25-10c.

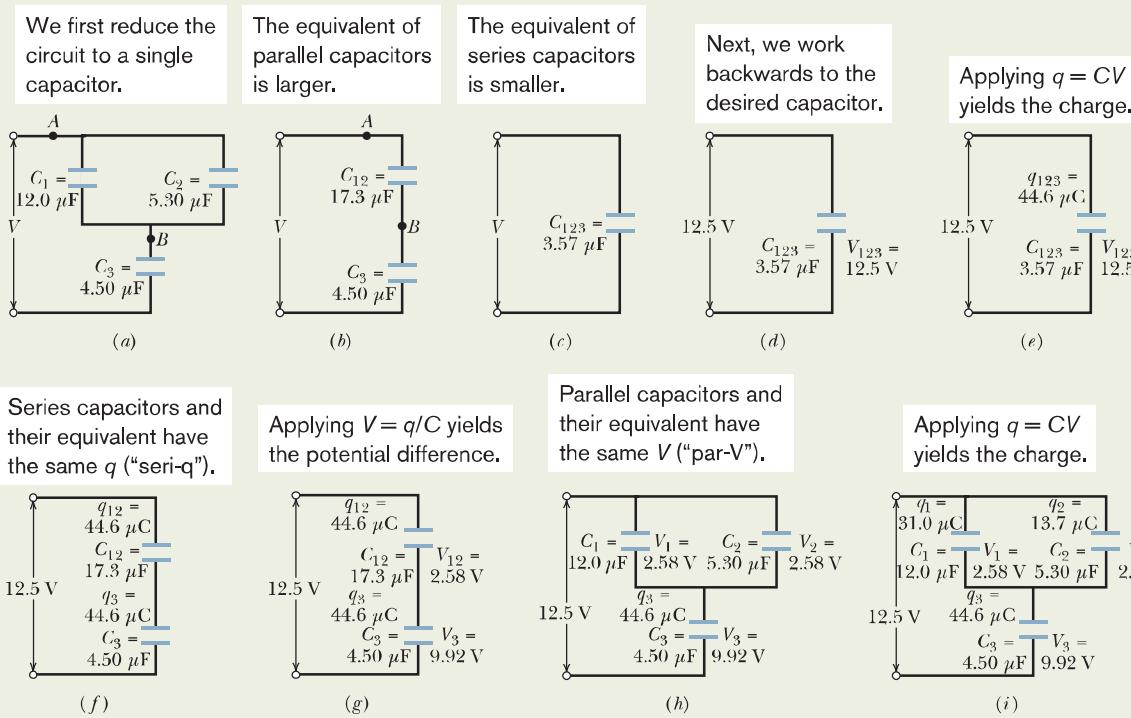

**Fig. 25-10** (a)–(d) Three capacitors are reduced to one equivalent capacitor. (e)–(i) Working backwards to get the charges.

From Eq. 25-20, we have

$$\begin{aligned}\frac{1}{C_{123}} &= \frac{1}{C_{12}} + \frac{1}{C_3} \\ &= \frac{1}{17.3 \mu\text{F}} + \frac{1}{4.50 \mu\text{F}} = 0.280 \mu\text{F}^{-1},\end{aligned}$$

from which

$$C_{123} = \frac{1}{0.280 \mu\text{F}^{-1}} = 3.57 \mu\text{F}. \quad (\text{Answer})$$

(b) The potential difference applied to the input terminals in Fig. 25-10a is  $V = 12.5$  V. What is the charge on  $C_1$ ?

#### KEY IDEAS

We now need to work backwards from the equivalent capacitance to get the charge on a particular capacitor. We have two techniques for such “backwards work”: (1) Seri-q: Series capacitors have the same charge as their equivalent capacitor. (2) Par-V: Parallel capacitors have the same potential difference as their equivalent capacitor.

**Working backwards:** To get the charge  $q_1$  on capacitor 1, we work backwards to that capacitor, starting with the equivalent capacitor 123. Because the given potential difference  $V (= 12.5$  V) is applied across the actual combination of three capacitors in Fig. 25-10a, it is also applied across  $C_{123}$  in Figs. 25-10d and e. Thus, Eq. 25-1 ( $q = CV$ ) gives us

$$q_{123} = C_{123}V = (3.57 \mu\text{F})(12.5 \text{ V}) = 44.6 \mu\text{C}.$$

The series capacitors 12 and 3 in Fig. 25-10b each have the same charge as their equivalent capacitor 123 (Fig. 25-10f). Thus, capacitor 12 has charge  $q_{12} = q_{123} = 44.6 \mu\text{C}$ . From Eq. 25-1 and Fig. 25-10g, the potential difference across capacitor 12 must be

$$V_{12} = \frac{q_{12}}{C_{12}} = \frac{44.6 \mu\text{C}}{17.3 \mu\text{F}} = 2.58 \text{ V}.$$

The parallel capacitors 1 and 2 each have the same potential difference as their equivalent capacitor 12 (Fig. 25-10h). Thus, capacitor 1 has potential difference  $V_1 = V_{12} = 2.58$  V, and, from Eq. 25-1 and Fig. 25-10i, the charge on capacitor 1 must be

$$\begin{aligned}q_1 &= C_1 V_1 = (12.0 \mu\text{F})(2.58 \text{ V}) \\ &= 31.0 \mu\text{C}. \quad (\text{Answer})\end{aligned}$$

#### Sample Problem

##### One capacitor charging up another capacitor

Capacitor 1, with  $C_1 = 3.55 \mu\text{F}$ , is charged to a potential difference  $V_0 = 6.30$  V, using a 6.30 V battery. The battery is then removed, and the capacitor is connected as in Fig. 25-11 to an uncharged capacitor 2, with  $C_2 = 8.95 \mu\text{F}$ . When switch S is closed, charge flows between the capacitors. Find the charge on each capacitor when equilibrium is reached.

#### KEY IDEAS

The situation here differs from the previous example because here an applied electric potential is *not* maintained across a combination of capacitors by a battery or some other source. Here, just after switch S is closed, the only applied electric potential is that of capacitor 1 on capacitor 2, and that potential is decreasing. Thus, the capacitors in Fig. 25-11 are not connected *in series*; and although they are drawn parallel, in this situation they are not *in parallel*.

As the electric potential across capacitor 1 decreases, that across capacitor 2 increases. Equilibrium is reached when the two potentials are equal because, with no potential difference between connected plates of the capacitors, there is no electric field within the connecting wires to move conduction electrons. The initial charge on capacitor 1 is then shared between the two capacitors.

**Calculations:** Initially, when capacitor 1 is connected to the battery, the charge it acquires is, from Eq. 25-1,

$$\begin{aligned}q_0 &= C_1 V_0 = (3.55 \times 10^{-6} \text{ F})(6.30 \text{ V}) \\ &= 22.365 \times 10^{-6} \text{ C}.\end{aligned}$$

When switch S in Fig. 25-11 is closed and capacitor 1 begins to charge capacitor 2, the electric potential and charge on capacitor 1 decrease and those on capacitor 2 increase until

$$V_1 = V_2 \quad (\text{equilibrium}).$$


From Eq. 25-1, we can rewrite this as

$$\frac{q_1}{C_1} = \frac{q_2}{C_2} \quad (\text{equilibrium}).$$

Because the total charge cannot magically change, the total after the transfer must be

$$q_1 + q_2 = q_0 \quad (\text{charge conservation});$$

After the switch is closed, charge is transferred until the potential differences match.

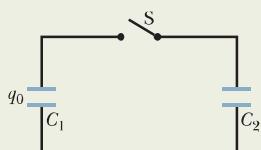

**Fig. 25-11** A potential difference  $V_0$  is applied to capacitor 1 and the charging battery is removed. Switch S is then closed so that the charge on capacitor 1 is shared with capacitor 2.

thus  $q_2 = q_0 - q_1$ .

We can now rewrite the second equilibrium equation as

$$\frac{q_1}{C_1} = \frac{q_0 - q_1}{C_2}.$$

Solving this for  $q_1$  and substituting given data, we find

$$q_1 = 6.35 \mu\text{C}. \quad (\text{Answer})$$

The rest of the initial charge ( $q_0 = 22.365 \mu\text{C}$ ) must be on capacitor 2:

$$q_2 = 16.0 \mu\text{C}. \quad (\text{Answer})$$



Additional examples, video, and practice available at WileyPLUS

## 25-5 Energy Stored in an Electric Field

Work must be done by an external agent to charge a capacitor. Starting with an uncharged capacitor, for example, imagine that—using “magic tweezers”—you remove electrons from one plate and transfer them one at a time to the other plate. The electric field that builds up in the space between the plates has a direction that tends to oppose further transfer. Thus, as charge accumulates on the capacitor plates, you have to do increasingly larger amounts of work to transfer additional electrons. In practice, this work is done not by “magic tweezers” but by a battery, at the expense of its store of chemical energy.

We visualize the work required to charge a capacitor as being stored in the form of electric potential energy  $U$  in the electric field between the plates. You can recover this energy at will, by discharging the capacitor in a circuit, just as you can recover the potential energy stored in a stretched bow by releasing the bow-string to transfer the energy to the kinetic energy of an arrow.

Suppose that, at a given instant, a charge  $q'$  has been transferred from one plate of a capacitor to the other. The potential difference  $V'$  between the plates at that instant will be  $q'/C$ . If an extra increment of charge  $dq'$  is then transferred, the increment of work required will be, from Eq. 24-7,

$$dW = V' dq' = \frac{q'}{C} dq'.$$

The work required to bring the total capacitor charge up to a final value  $q$  is

$$W = \int dW = \frac{1}{C} \int_0^q q' dq' = \frac{q^2}{2C}.$$

This work is stored as potential energy  $U$  in the capacitor, so that

$$U = \frac{q^2}{2C} \quad (\text{potential energy}). \quad (25-21)$$

From Eq. 25-1, we can also write this as

$$U = \frac{1}{2} CV^2 \quad (\text{potential energy}). \quad (25-22)$$

Equations 25-21 and 25-22 hold no matter what the geometry of the capacitor is.

To gain some physical insight into energy storage, consider two parallel-plate capacitors that are identical except that capacitor 1 has twice the plate separation of capacitor 2. Then capacitor 1 has twice the volume between its plates and also, from Eq. 25-9, half the capacitance of capacitor 2. Equation 25-4 tells us that if both capacitors have the same charge  $q$ , the electric fields between their plates are identical. And Eq. 25-21 tells us that capacitor 1 has twice the stored potential energy of capacitor 2. Thus, of two otherwise identical capacitors with the same charge and same electric field, the one with twice the volume between its plates has twice the stored potential energy. Arguments like this tend to verify our earlier assumption:



The potential energy of a charged capacitor may be viewed as being stored in the electric field between its plates.

## Explosions in Airborne Dust

As we discussed in Section 24-12, making contact with certain materials, such as clothing, carpets, and even playground slides, can leave you with a significant electrical potential. You might become painfully aware of that potential if a spark leaps between you and a grounded object, such as a faucet. In many industries involving the production and transport of powder, such as in the cosmetic and food industries, such a spark can be disastrous. Although the powder in bulk may not burn at all, when individual powder grains are airborne and thus surrounded by oxygen, they can burn so fiercely that a cloud of the grains burns as an explosion. Safety engineers cannot eliminate all possible sources of sparks in the powder industries. Instead, they attempt to keep the amount of energy available in the sparks below the threshold value  $U_t$  ( $\approx 150$  mJ) typically required to ignite airborne grains.

Suppose a person becomes charged by contact with various surfaces as he walks through an airborne powder. We can roughly model the person as a spherical capacitor of radius  $R = 1.8$  m. From Eq. 25-18 ( $C = 4\pi\epsilon_0 R$ ) and Eq. 25-22 ( $U = \frac{1}{2}CV^2$ ), we see that the energy of the capacitor is

$$U = \frac{1}{2}(4\pi\epsilon_0 R)V^2.$$

From this we see that the threshold energy corresponds to a potential of

$$\begin{aligned} V &= \sqrt{\frac{2U_t}{4\pi\epsilon_0 R}} = \sqrt{\frac{2(150 \times 10^{-3} \text{ J})}{4\pi(8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2)(1.8 \text{ m})}} \\ &= 3.9 \times 10^4 \text{ V}. \end{aligned}$$

Safety engineers attempt to keep the potential of the personnel below this level by “bleeding” off the charge through, say, a conducting floor.



## Energy Density

In a parallel-plate capacitor, neglecting fringing, the electric field has the same value at all points between the plates. Thus, the **energy density**  $u$ —that is, the potential energy per unit volume between the plates—should also be uniform. We can find  $u$  by dividing the total potential energy by the volume  $Ad$  of the space between the plates. Using Eq. 25-22, we obtain

$$u = \frac{U}{Ad} = \frac{CV^2}{2Ad}. \quad (25-23)$$

With Eq. 25-9 ( $C = \epsilon_0 A/d$ ), this result becomes

$$u = \frac{1}{2}\epsilon_0 \left(\frac{V}{d}\right)^2. \quad (25-24)$$

However, from Eq. 24-42 ( $E = -\Delta V/\Delta s$ ),  $V/d$  equals the electric field magnitude  $E$ ; so

$$u = \frac{1}{2}\epsilon_0 E^2 \quad (\text{energy density}). \quad (25-25)$$

Although we derived this result for the special case of an electric field of a parallel-plate capacitor, it holds generally, whatever may be the source of the electric field. If an electric field  $\vec{E}$  exists at any point in space, we can think of that point as a site of electric potential energy with a density (amount per unit volume) given by Eq. 25-25.

**Sample Problem****Potential energy and energy density of an electric field**

An isolated conducting sphere whose radius  $R$  is 6.85 cm has a charge  $q = 1.25 \text{ nC}$ .

(a) How much potential energy is stored in the electric field of this charged conductor?

**KEY IDEAS**

(1) An isolated sphere has capacitance given by Eq. 25-18 ( $C = 4\pi\epsilon_0 R$ ). (2) The energy  $U$  stored in a capacitor depends on the capacitor's charge  $q$  and capacitance  $C$  according to Eq. 25-21 ( $U = q^2/2C$ ).

**Calculation:** Substituting  $C = 4\pi\epsilon_0 R$  into Eq. 25-21 gives us

$$\begin{aligned} U &= \frac{q^2}{2C} = \frac{q^2}{8\pi\epsilon_0 R} \\ &= \frac{(1.25 \times 10^{-9} \text{ C})^2}{(8\pi)(8.85 \times 10^{-12} \text{ F/m})(0.0685 \text{ m})} \\ &= 1.03 \times 10^{-7} \text{ J} = 103 \text{ nJ.} \quad (\text{Answer}) \end{aligned}$$

(b) What is the energy density at the surface of the sphere?

**KEY IDEA**

The density  $u$  of the energy stored in an electric field depends on the magnitude  $E$  of the field, according to Eq. 25-25 ( $u = \frac{1}{2}\epsilon_0 E^2$ ).

**Calculations:** Here we must first find  $E$  at the surface of the sphere, as given by Eq. 23-15:

$$E = \frac{1}{4\pi\epsilon_0} \frac{q}{R^2}.$$

The energy density is then

$$\begin{aligned} u &= \frac{1}{2}\epsilon_0 E^2 = \frac{q^2}{32\pi^2\epsilon_0 R^4} \\ &= \frac{(1.25 \times 10^{-9} \text{ C})^2}{(32\pi^2)(8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2)(0.0685 \text{ m})^4} \\ &= 2.54 \times 10^{-5} \text{ J/m}^3 = 25.4 \mu\text{J/m}^3. \quad (\text{Answer}) \end{aligned}$$



Additional examples, video, and practice available at WileyPLUS

**25-6 Capacitor with a Dielectric**

If you fill the space between the plates of a capacitor with a *dielectric*, which is an insulating material such as mineral oil or plastic, what happens to the capacitance? Michael Faraday—to whom the whole concept of capacitance is largely due and for whom the SI unit of capacitance is named—first looked into this matter in 1837. Using simple equipment much like that shown in Fig. 25-12, he found that the capacitance *increased* by a numerical factor  $\kappa$ , which he called the **dielectric constant** of the insulating material. Table 25-1 shows some dielectric materials and their dielectric constants. The dielectric constant of a vacuum is unity by definition. Because air is mostly empty space, its measured dielectric constant is only slightly greater than unity. Even common paper can significantly

**Fig. 25-12** The simple electrostatic apparatus used by Faraday. An assembled apparatus (second from left) forms a spherical capacitor consisting of a central brass ball and a concentric brass shell. Faraday placed dielectric materials in the space between the ball and the shell. (The Royal Institute, England/Bridgeman Art Library/NY)


**Table 25-1**

Some Properties of Dielectrics<sup>a</sup>

Material	Dielectric Constant $\kappa$	Dielectric Strength (kV/mm)
Air (1 atm)	1.00054	3
Polystyrene	2.6	24
Paper	3.5	16
Transformer oil	4.5	
Pyrex	4.7	14
Ruby mica	5.4	
Porcelain	6.5	
Silicon	12	
Germanium	16	
Ethanol	25	
Water (20°C)	80.4	
Water (25°C)	78.5	
Titania ceramic	130	
Strontium titanate	310	8

For a vacuum,  $\kappa = \text{unity}$ .

<sup>a</sup>Measured at room temperature, except for the water.

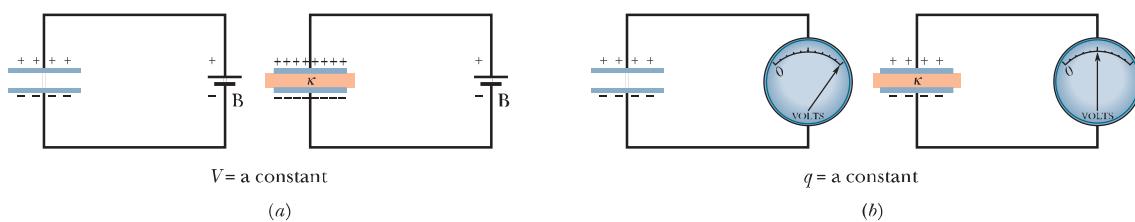

**Fig. 25-13** (a) If the potential difference between the plates of a capacitor is maintained, as by battery B, the effect of a dielectric is to increase the charge on the plates. (b) If the charge on the capacitor plates is maintained, as in this case, the effect of a dielectric is to reduce the potential difference between the plates. The scale shown is that of a *potentiometer*, a device used to measure potential difference (here, between the plates). A capacitor cannot discharge through a potentiometer.

increase the capacitance of a capacitor, and some materials, such as strontium titanate, can increase the capacitance by more than two orders of magnitude.

Another effect of the introduction of a dielectric is to limit the potential difference that can be applied between the plates to a certain value  $V_{\max}$ , called the *breakdown potential*. If this value is substantially exceeded, the dielectric material will break down and form a conducting path between the plates. Every dielectric material has a characteristic *dielectric strength*, which is the maximum value of the electric field that it can tolerate without breakdown. A few such values are listed in Table 25-1.

As we discussed just after Eq. 25-18, the capacitance of any capacitor can be written in the form

$$C = \epsilon_0 \mathcal{L}, \quad (25-26)$$

in which  $\mathcal{L}$  has the dimension of length. For example,  $\mathcal{L} = A/d$  for a parallel-plate capacitor. Faraday's discovery was that, with a dielectric completely filling the space between the plates, Eq. 25-26 becomes

$$C = \kappa \epsilon_0 \mathcal{L} = \kappa C_{\text{air}}, \quad (25-27)$$

where  $C_{\text{air}}$  is the value of the capacitance with only air between the plates. For example, if we fill a capacitor with strontium titanate, with a dielectric constant of 310, we multiply the capacitance by 310.

Figure 25-13 provides some insight into Faraday's experiments. In Fig. 25-13a the battery ensures that the potential difference  $V$  between the plates will remain constant. When a dielectric slab is inserted between the plates, the charge  $q$  on the plates increases by a factor of  $\kappa$ ; the additional charge is delivered to the capacitor plates by the battery. In Fig. 25-13b there is no battery, and therefore the charge  $q$  must remain constant when the dielectric slab is inserted; then the potential difference  $V$  between the plates decreases by a factor of  $\kappa$ . Both these observations are consistent (through the relation  $q = CV$ ) with the increase in capacitance caused by the dielectric.

Comparison of Eqs. 25-26 and 25-27 suggests that the effect of a dielectric can be summed up in more general terms:



In a region completely filled by a dielectric material of dielectric constant  $\kappa$ , all electrostatic equations containing the permittivity constant  $\epsilon_0$  are to be modified by replacing  $\epsilon_0$  with  $\kappa \epsilon_0$ .

Thus, the magnitude of the electric field produced by a point charge inside a dielectric is given by this modified form of Eq. 23-15:

$$E = \frac{1}{4\pi\kappa\epsilon_0} \frac{q}{r^2}. \quad (25-28)$$

Also, the expression for the electric field just outside an isolated conductor immersed in a dielectric (see Eq. 23-11) becomes

$$E = \frac{\sigma}{\kappa\epsilon_0}. \quad (25-29)$$

Because  $\kappa$  is always greater than unity, both these equations show that *for a fixed distribution of charges, the effect of a dielectric is to weaken the electric field that would otherwise be present*.

**Sample Problem****Work and energy when a dielectric is inserted into a capacitor**

A parallel-plate capacitor whose capacitance  $C$  is 13.5 pF is charged by a battery to a potential difference  $V = 12.5$  V between its plates. The charging battery is now disconnected, and a porcelain slab ( $\kappa = 6.50$ ) is slipped between the plates.

(a) What is the potential energy of the capacitor before the slab is inserted?

**KEY IDEA**

We can relate the potential energy  $U_i$  of the capacitor to the capacitance  $C$  and either the potential  $V$  (with Eq. 25-22) or the charge  $q$  (with Eq. 25-21):

$$U_i = \frac{1}{2}CV^2 = \frac{q^2}{2C}$$

**Calculation:** Because we are given the initial potential  $V$  ( $= 12.5$  V), we use Eq. 25-22 to find the initial stored energy:

$$\begin{aligned} U_i &= \frac{1}{2}CV^2 = \frac{1}{2}(13.5 \times 10^{-12} \text{ F})(12.5 \text{ V})^2 \\ &= 1.055 \times 10^{-9} \text{ J} = 1055 \text{ pJ} \approx 1100 \text{ pJ}. \quad (\text{Answer}) \end{aligned}$$

(b) What is the potential energy of the capacitor–slab device after the slab is inserted?

**KEY IDEA**

Because the battery has been disconnected, the charge on the capacitor cannot change when the dielectric is inserted. However, the potential *does* change.

**Calculations:** Thus, we must now use Eq. 25-21 to write the final potential energy  $U_f$ , but now that the slab is within the capacitor, the capacitance is  $\kappa C$ . We then have

$$\begin{aligned} U_f &= \frac{q^2}{2\kappa C} = \frac{U_i}{\kappa} = \frac{1055 \text{ pJ}}{6.50} \\ &= 162 \text{ pJ} \approx 160 \text{ pJ}. \quad (\text{Answer}) \end{aligned}$$

When the slab is introduced, the potential energy decreases by a factor of  $\kappa$ .

The “missing” energy, in principle, would be apparent to the person who introduced the slab. The capacitor would exert a tiny tug on the slab and would do work on it, in amount

$$W = U_i - U_f = (1055 - 162) \text{ pJ} = 893 \text{ pJ}.$$

If the slab were allowed to slide between the plates with no restraint and if there were no friction, the slab would oscillate back and forth between the plates with a (constant) mechanical energy of 893 pJ, and this system energy would transfer back and forth between kinetic energy of the moving slab and potential energy stored in the electric field.




Additional examples, video, and practice available at WileyPLUS


## 25-7 Dielectrics: An Atomic View

What happens, in atomic and molecular terms, when we put a dielectric in an electric field? There are two possibilities, depending on the type of molecule:


1. **Polar dielectrics.** The molecules of some dielectrics, like water, have permanent electric dipole moments. In such materials (called *polar dielectrics*), the electric dipoles tend to line up with an external electric field as in Fig. 25-14. Because the molecules are continuously jostling each other as a result of their random thermal motion, this alignment is not complete, but it becomes more complete as the magnitude of the applied field is increased (or as the temperature, and thus the jostling, are decreased). The alignment of the electric dipoles produces an electric field that is directed opposite the applied field and is smaller in magnitude.

**Fig. 25-14** (a) Molecules with a permanent electric dipole moment, showing their random orientation in the absence of an external electric field. (b) An electric field is applied, producing partial alignment of the dipoles. Thermal agitation prevents complete alignment.

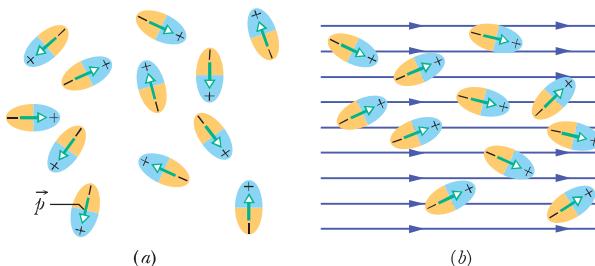


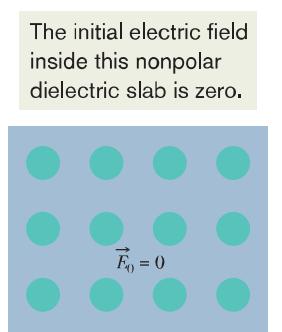

(a)

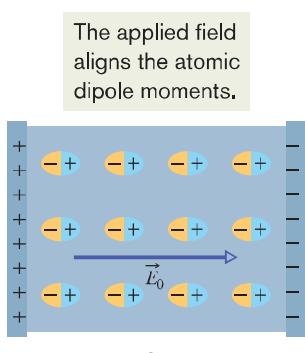

(b)

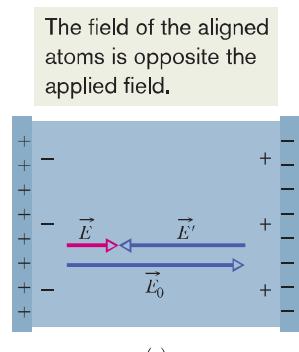

(c)

**Fig. 25-15** (a) A nonpolar dielectric slab. The circles represent the electrically neutral atoms within the slab. (b) An electric field is applied via charged capacitor plates; the field slightly stretches the atoms, separating the centers of positive and negative charge. (c) The separation produces surface charges on the slab faces. These charges set up a field  $\vec{E}'$ , which opposes the applied field  $\vec{E}_0$ . The resultant field  $\vec{E}$  inside the dielectric (the vector sum of  $\vec{E}_0$  and  $\vec{E}'$ ) has the same direction as  $\vec{E}_0$  but a smaller magnitude.

**2. Nonpolar dielectrics.** Regardless of whether they have permanent electric dipole moments, molecules acquire dipole moments by induction when placed in an external electric field. In Section 24-8 (see Fig. 24-11), we saw that this occurs because the external field tends to “stretch” the molecules, slightly separating the centers of negative and positive charge.

Figure 25-15a shows a nonpolar dielectric slab with no external electric field applied. In Fig. 25-15b, an electric field  $\vec{E}_0$  is applied via a capacitor, whose plates are charged as shown. The result is a slight separation of the centers of the positive and negative charge distributions within the slab, producing positive charge on one face of the slab (due to the positive ends of dipoles there) and negative charge on the opposite face (due to the negative ends of dipoles there). The slab as a whole remains electrically neutral and—within the slab—there is no excess charge in any volume element.

Figure 25-15c shows that the induced surface charges on the faces produce an electric field  $\vec{E}'$  in the direction opposite that of the applied electric field  $\vec{E}_0$ . The resultant field  $\vec{E}$  inside the dielectric (the vector sum of fields  $\vec{E}_0$  and  $\vec{E}'$ ) has the direction of  $\vec{E}_0$  but is smaller in magnitude.

Both the field  $\vec{E}'$  produced by the surface charges in Fig. 25-15c and the electric field produced by the permanent electric dipoles in Fig. 25-14 act in the same way—they oppose the applied field  $\vec{E}$ . Thus, the effect of both polar and nonpolar dielectrics is to weaken any applied field within them, as between the plates of a capacitor.

## 25-8 Dielectrics and Gauss' Law

In our discussion of Gauss' law in Chapter 23, we assumed that the charges existed in a vacuum. Here we shall see how to modify and generalize that law if dielectric materials, such as those listed in Table 25-1, are present. Figure 25-16 shows a parallel-plate capacitor of plate area  $A$ , both with and without a dielectric. We assume that the charge  $q$  on the plates is the same in both situations. Note that the field between the plates induces charges on the faces of the dielectric by one of the methods described in Section 25-7.

For the situation of Fig. 25-16a, without a dielectric, we can find the electric field  $\vec{E}_0$  between the plates as we did in Fig. 25-5: We enclose the charge  $+q$  on the top plate with a Gaussian surface and then apply Gauss' law. Letting  $E_0$  represent the magnitude of the field, we find


$$\epsilon_0 \oint \vec{E} \cdot d\vec{A} = \epsilon_0 EA = q, \quad (25-30)$$

or

$$E_0 = \frac{q}{\epsilon_0 A}. \quad (25-31)$$

In Fig. 25-16b, with the dielectric in place, we can find the electric field between the plates (and within the dielectric) by using the same Gaussian surface. However, now the surface encloses two types of charge: It still encloses

**Fig. 25-16** A parallel-plate capacitor (a) without and (b) with a dielectric slab inserted. The charge  $q$  on the plates is assumed to be the same in both cases.

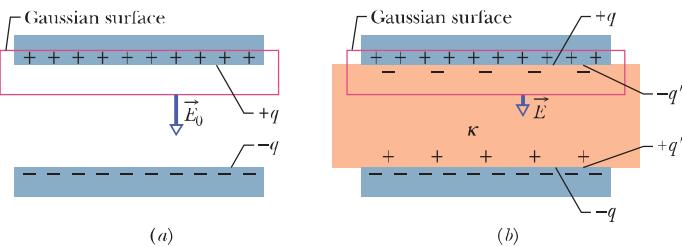

charge  $+q$  on the top plate, but it now also encloses the induced charge  $-q'$  on the top face of the dielectric. The charge on the conducting plate is said to be *free charge* because it can move if we change the electric potential of the plate; the induced charge on the surface of the dielectric is not free charge because it cannot move from that surface.

The net charge enclosed by the Gaussian surface in Fig. 25-16b is  $q - q'$ , so Gauss' law now gives

$$\varepsilon_0 \oint \vec{E} \cdot d\vec{A} = \varepsilon_0 E A = q - q', \quad (25-32)$$

or

$$E = \frac{q - q'}{\varepsilon_0 A}. \quad (25-33)$$

The effect of the dielectric is to weaken the original field  $E_0$  by a factor of  $\kappa$ ; so we may write

$$E = \frac{E_0}{\kappa} = \frac{q}{\kappa \varepsilon_0 A}. \quad (25-34)$$

Comparison of Eqs. 25-33 and 25-34 shows that

$$q - q' = \frac{q}{\kappa}. \quad (25-35)$$

Equation 25-35 shows correctly that the magnitude  $q'$  of the induced surface charge is less than that of the free charge  $q$  and is zero if no dielectric is present (because then  $\kappa = 1$  in Eq. 25-35).

By substituting for  $q - q'$  from Eq. 25-35 in Eq. 25-32, we can write Gauss' law in the form

$$\varepsilon_0 \oint \kappa \vec{E} \cdot d\vec{A} = q \quad (\text{Gauss' law with dielectric}). \quad (25-36)$$

This equation, although derived for a parallel-plate capacitor, is true generally and is the most general form in which Gauss' law can be written. Note:

1. The flux integral now involves  $\kappa \vec{E}$ , not just  $\vec{E}$ . (The vector  $\varepsilon_0 \kappa \vec{E}$  is sometimes called the *electric displacement*  $\vec{D}$ , so that Eq. 25-36 can be written in the form  $\oint \vec{D} \cdot d\vec{A} = q$ .)
2. The charge  $q$  enclosed by the Gaussian surface is now taken to be the *free charge only*. The induced surface charge is deliberately ignored on the right side of Eq. 25-36, having been taken fully into account by introducing the dielectric constant  $\kappa$  on the left side.
3. Equation 25-36 differs from Eq. 23-7, our original statement of Gauss' law, only in that  $\varepsilon_0$  in the latter equation has been replaced by  $\kappa \varepsilon_0$ . We keep  $\kappa$  inside the integral of Eq. 25-36 to allow for cases in which  $\kappa$  is not constant over the entire Gaussian surface.

### Sample Problem

#### Dielectric partially filling the gap in a capacitor

Figure 25-17 shows a parallel-plate capacitor of plate area  $A$  and plate separation  $d$ . A potential difference  $V_0$  is applied between the plates by connecting a battery between them. The battery is then disconnected, and a dielectric slab of thickness  $b$  and dielectric constant  $\kappa$  is placed between the plates as shown. Assume  $A = 115 \text{ cm}^2$ ,  $d = 1.24 \text{ cm}$ ,  $V_0 = 85.5 \text{ V}$ ,  $b = 0.780 \text{ cm}$ , and  $\kappa = 2.61$ .

- (a) What is the capacitance  $C_0$  before the dielectric slab is inserted?

**Calculation:** From Eq. 25-9 we have

$$\begin{aligned} C_0 &= \frac{\varepsilon_0 A}{d} = \frac{(8.85 \times 10^{-12} \text{ F/m})(115 \times 10^{-4} \text{ m}^2)}{1.24 \times 10^{-2} \text{ m}} \\ &= 8.21 \times 10^{-12} \text{ F} = 8.21 \text{ pF}. \end{aligned} \quad (\text{Answer})$$

(b) What free charge appears on the plates?

**Calculation:** From Eq. 25-1,

$$q = C_0 V_0 = (8.21 \times 10^{-12} \text{ F})(85.5 \text{ V}) \\ = 7.02 \times 10^{-10} \text{ C} = 702 \text{ pC.} \quad (\text{Answer})$$

Because the battery was disconnected before the slab was inserted, the free charge is unchanged.

(c) What is the electric field  $E_0$  in the gaps between the plates and the dielectric slab?

#### KEY IDEA

We need to apply Gauss' law, in the form of Eq. 25-36, to Gaussian surface I in Fig. 25-17.

**Calculations:** That surface passes through the gap, and so it encloses *only* the free charge on the upper capacitor plate. Electric field pierces only the bottom of the Gaussian surface. Because there the area vector  $d\vec{A}$  and the field vector  $\vec{E}_0$  are both directed downward, the dot product in Eq. 25-36 becomes

$$\vec{E}_0 \cdot d\vec{A} = E_0 dA \cos 0^\circ = E_0 dA.$$

Equation 25-36 then becomes

$$\epsilon_0 \kappa E_0 \oint dA = q.$$

The integration now simply gives the surface area  $A$  of the plate. Thus, we obtain

$$\epsilon_0 \kappa E_0 A = q,$$

or

$$E_0 = \frac{q}{\epsilon_0 \kappa A}.$$

We must put  $\kappa = 1$  here because Gaussian surface I does not pass through the dielectric. Thus, we have

$$E_0 = \frac{q}{\epsilon_0 \kappa A} = \frac{7.02 \times 10^{-10} \text{ C}}{(8.85 \times 10^{-12} \text{ F/m})(1)(115 \times 10^{-4} \text{ m}^2)} \\ = 6900 \text{ V/m} = 6.90 \text{ kV/m.} \quad (\text{Answer})$$

Note that the value of  $E_0$  does not change when the slab is introduced because the amount of charge enclosed by Gaussian surface I in Fig. 25-17 does not change.

(d) What is the electric field  $E_1$  in the dielectric slab?


#### KEY IDEA

Now we apply Gauss' law in the form of Eq. 25-36 to Gaussian surface II in Fig. 25-17.

**Calculations:** That surface encloses free charge  $-q$  and induced charge  $+q'$ , but we ignore the latter when we use Eq. 25-36. We find

$$\epsilon_0 \oint \kappa \vec{E}_1 \cdot d\vec{A} = -\epsilon_0 \kappa E_1 A = -q. \quad (25-37)$$

**Fig. 25-17**

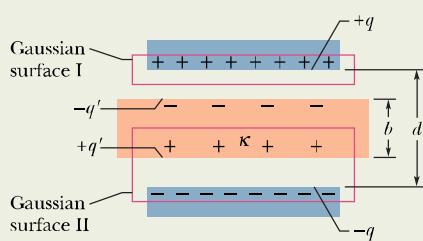

The first minus sign in this equation comes from the dot product  $\vec{E}_1 \cdot d\vec{A}$  along the top of the Gaussian surface because now the field vector  $\vec{E}_1$  is directed downward and the area vector  $d\vec{A}$  (which, as always, points outward from the interior of a closed Gaussian surface) is directed upward. With  $180^\circ$  between the vectors, the dot product is negative. Now  $\kappa = 2.61$ . Thus, Eq. 25-37 gives us

$$E_1 = \frac{q}{\epsilon_0 \kappa A} = \frac{E_0}{\kappa} = \frac{6.90 \text{ kV/m}}{2.61} \\ = 2.64 \text{ kV/m.} \quad (\text{Answer})$$

(e) What is the potential difference  $V$  between the plates after the slab has been introduced?

#### KEY IDEA

We find  $V$  by integrating along a straight line directly from the bottom plate to the top plate.

**Calculation:** Within the dielectric, the path length is  $b$  and the electric field is  $E_1$ . Within the two gaps above and below the dielectric, the total path length is  $d - b$  and the electric field is  $E_0$ . Equation 25-6 then yields

$$V = \int_{-}^{+} E ds = E_0(d - b) + E_1 b \\ = (6900 \text{ V/m})(0.0124 \text{ m} - 0.00780 \text{ m}) \\ + (2640 \text{ V/m})(0.00780 \text{ m}) \\ = 52.3 \text{ V.} \quad (\text{Answer})$$

This is less than the original potential difference of 85.5 V.

(f) What is the capacitance with the slab in place between the plates of the capacitor?

#### KEY IDEA

The capacitance  $C$  is related to the free charge  $q$  and the potential difference  $V$  via Eq. 25-1.

**Calculation:** Taking  $q$  from (b) and  $V$  from (e), we have

$$C = \frac{q}{V} = \frac{7.02 \times 10^{-10} \text{ C}}{52.3 \text{ V}} \\ = 1.34 \times 10^{-11} \text{ F} = 13.4 \text{ pF.} \quad (\text{Answer})$$

This is greater than the original capacitance of 8.21 pF.



Additional examples, video, and practice available at WileyPLUS

## REVIEW &amp; SUMMARY

**Capacitor; Capacitance** A **capacitor** consists of two isolated conductors (the *plates*) with charges  $+q$  and  $-q$ . Its **capacitance**  $C$  is defined from

$$q = CV, \quad (25-1)$$

where  $V$  is the potential difference between the plates.

**Determining Capacitance** We generally determine the capacitance of a particular capacitor configuration by (1) assuming a charge  $q$  to have been placed on the plates, (2) finding the electric field  $\vec{E}$  due to this charge, (3) evaluating the potential difference  $V$ , and (4) calculating  $C$  from Eq. 25-1. Some specific results are the following:

A *parallel-plate capacitor* with flat parallel plates of area  $A$  and spacing  $d$  has capacitance

$$C = \frac{\epsilon_0 A}{d}. \quad (25-9)$$

A *cylindrical capacitor* (two long coaxial cylinders) of length  $L$  and radii  $a$  and  $b$  has capacitance

$$C = 2\pi\epsilon_0 \frac{L}{\ln(b/a)}. \quad (25-14)$$

A *spherical capacitor* with concentric spherical plates of radii  $a$  and  $b$  has capacitance

$$C = 4\pi\epsilon_0 \frac{ab}{b-a}. \quad (25-17)$$

An *isolated sphere* of radius  $R$  has capacitance

$$C = 4\pi\epsilon_0 R. \quad (25-18)$$

**Capacitors in Parallel and in Series** The **equivalent capacitances**  $C_{eq}$  of combinations of individual capacitors connected in **parallel** and in **series** can be found from

$$C_{eq} = \sum_{j=1}^n C_j \quad (n \text{ capacitors in parallel}) \quad (25-19)$$

and  $\frac{1}{C_{eq}} = \sum_{j=1}^n \frac{1}{C_j} \quad (n \text{ capacitors in series}). \quad (25-20)$

Equivalent capacitances can be used to calculate the capacitances of more complicated series-parallel combinations.

**Potential Energy and Energy Density** The **electric potential energy**  $U$  of a charged capacitor,

$$U = \frac{q^2}{2C} = \frac{1}{2}CV^2, \quad (25-21, 25-22)$$

is equal to the work required to charge the capacitor. This energy can be associated with the capacitor's electric field  $\vec{E}$ . By extension we can associate stored energy with any electric field. In vacuum, the **energy density**  $u$ , or potential energy per unit volume, within an electric field of magnitude  $E$  is given by

$$u = \frac{1}{2}\epsilon_0 E^2. \quad (25-25)$$

**Capacitance with a Dielectric** If the space between the plates of a capacitor is completely filled with a dielectric material, the capacitance  $C$  is increased by a factor  $\kappa$ , called the **dielectric constant**, which is characteristic of the material. In a region that is completely filled by a dielectric, all electrostatic equations containing  $\epsilon_0$  must be modified by replacing  $\epsilon_0$  with  $\kappa\epsilon_0$ .

The effects of adding a dielectric can be understood physically in terms of the action of an electric field on the permanent or induced electric dipoles in the dielectric slab. The result is the formation of induced charges on the surfaces of the dielectric, which results in a weakening of the field within the dielectric for a given amount of free charge on the plates.

**Gauss' Law with a Dielectric** When a dielectric is present, Gauss' law may be generalized to

$$\epsilon_0 \oint \kappa \vec{E} \cdot d\vec{A} = q. \quad (25-36)$$

Here  $q$  is the free charge; any induced surface charge is accounted for by including the dielectric constant  $\kappa$  inside the integral.

## QUESTIONS

- 1 Figure 25-18 shows plots of charge versus potential difference for three parallel-plate capacitors that have the plate areas and separations given in the table. Which plot goes with which capacitor?

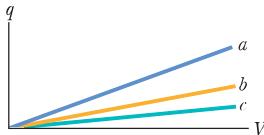


Fig. 25-18 Question 1.

Capacitor	Area	Separation
1	$A$	$d$
2	$2A$	$d$
3	$A$	$2d$

- 2 What is  $C_{eq}$  of three capacitors, each of capacitance  $C$ , if they are connected to a battery (a) in series with one another and (b) in parallel? (c) In which arrangement is there more charge on the equivalent capacitance?

- 3 (a) In Fig. 25-19a, are capacitors 1 and 3 in series? (b) In the same figure, are capacitors 1 and 2 in parallel? (c) Rank the equivalent capacitances of the four circuits shown in Fig. 25-19, greatest first.

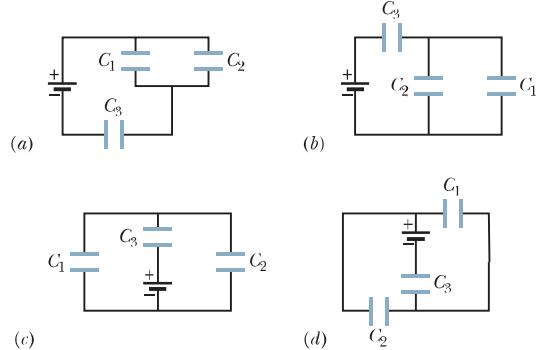


Fig. 25-19 Question 3.

- 4 Figure 25-20 shows three circuits, each consisting of a switch and two capacitors, initially charged as indicated (top plate positive). After the switches have been closed, in which circuit (if any) will the charge on the left-hand capacitor (a) increase, (b) decrease, and (c) remain the same?

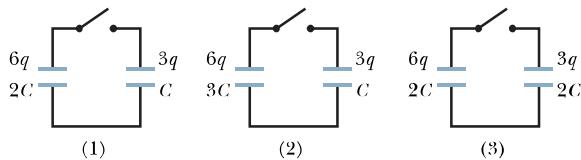


Fig. 25-20 Question 4.

- 5 Initially, a single capacitance  $C_1$  is wired to a battery. Then capacitance  $C_2$  is added in parallel. Are (a) the potential difference across  $C_1$  and (b) the charge  $q_1$  on  $C_1$  now more than, less than, or the same as previously? (c) Is the equivalent capacitance  $C_{12}$  of  $C_1$  and  $C_2$  more than, less than, or equal to  $C_1$ ? (d) Is the charge stored on  $C_1$  and  $C_2$  together more than, less than, or equal to the charge stored previously on  $C_1$ ?

- 6 Repeat Question 5 for  $C_2$  added in series rather than in parallel.  
7 For each circuit in Fig. 25-21, are the capacitors connected in series, in parallel, or in neither mode?

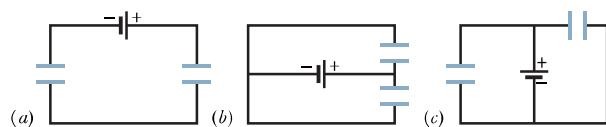


Fig. 25-21 Question 7.

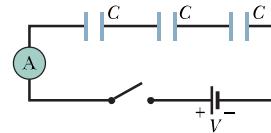


Fig. 25-22 Question 8.

- 8 Figure 25-22 shows an open switch, a battery of potential difference  $V$ , a current-measuring meter A, and three identical uncharged capacitors of capacitance  $C$ . When the switch is closed and the circuit reaches equilibrium, what are (a) the potential difference across each capacitor and (b) the charge on the left plate of each capacitor? (c) During charging, what net charge passes through the meter?

- 9 A parallel-plate capacitor is connected to a battery of electric potential difference  $V$ . If the plate separation is decreased, do the following quantities increase, decrease, or remain the same: (a) the capacitor's capacitance, (b) the potential difference across the capacitor, (c) the charge on the capacitor, (d) the energy stored by the capacitor, (e) the magnitude of the electric field between the plates, and (f) the energy density of that electric field?

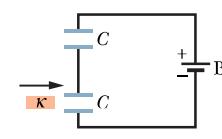


Fig. 25-19 Question 10.

- 10 When a dielectric slab is inserted between the plates of one of the two identical capacitors in Fig. 25-23, do the following properties of that capacitor increase, decrease, or remain the same: (a) capacitance, (b) charge, (c) potential difference, and (d) potential energy? (e) How about the same properties of the other capacitor?

- 11 You are to connect capacitances  $C_1$  and  $C_2$ , with  $C_1 > C_2$ , to a battery, first individually, then in series, and then in parallel. Rank those arrangements according to the amount of charge stored, greatest first.



## PROBLEMS



Tutoring problem available (at instructor's discretion) in WileyPLUS and WebAssign



Worked-out solution available in Student Solutions Manual



Number of dots indicates level of problem difficulty

Additional information available in *The Flying Circus of Physics* and at flyingcircusofphysics.com

WWW Worked-out solution is at

ILW Interactive solution is at

<http://www.wiley.com/college/halliday>**sec. 25-2 Capacitance**

- 1 The two metal objects in Fig. 25-24 have net charges of  $+70 \text{ pC}$  and  $-70 \text{ pC}$ , which result in a  $20 \text{ V}$  potential difference between them. (a) What is the capacitance of the system? (b) If the charges are changed to  $+200 \text{ pC}$  and  $-200 \text{ pC}$ , what does the capacitance become? (c) What does the potential difference become?



Fig. 25-24 Problem 1.

- 2 The capacitor in Fig. 25-25 has a capacitance of  $25 \mu\text{F}$  and is initially uncharged. The battery provides a potential difference of  $120 \text{ V}$ . After switch S is closed, how much charge will pass through it?

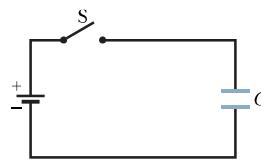


Fig. 25-25 Problem 2.

**sec. 25-3 Calculating the Capacitance**

- 3 **SSM** A parallel-plate capacitor has circular plates of  $8.20 \text{ cm}$  radius and  $1.30 \text{ mm}$  separation. (a) Calculate the capacitance. (b) Find the charge for a potential difference of  $120 \text{ V}$ .

- 4 The plates of a spherical capacitor have radii  $38.0 \text{ mm}$  and  $40.0 \text{ mm}$ . (a) Calculate the capacitance. (b) What must be the plate area of a parallel-plate capacitor with the same plate separation and capacitance?

- 5 What is the capacitance of a drop that results when two mercury spheres, each of radius  $R = 2.00 \text{ mm}$ , merge?

- 6 You have two flat metal plates, each of area  $1.00 \text{ m}^2$ , with which to construct a parallel-plate capacitor. (a) If the capacitance of the device is to be  $1.00 \text{ F}$ , what must be the separation between the plates? (b) Could this capacitor actually be constructed?

- 7 If an uncharged parallel-plate capacitor (capacitance  $C$ ) is connected to a battery, one plate becomes negatively charged as electrons move to the plate face (area  $A$ ). In Fig. 25-26, the depth  $d$  from which the electrons come in the plate in a particular capacitor is plotted against a range of values for the

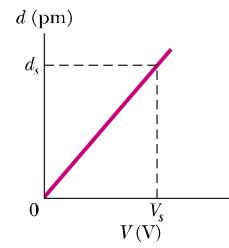



Fig. 25-26 Problem 7.

potential difference  $V$  of the battery. The density of conduction electrons in the copper plates is  $8.49 \times 10^{28}$  electrons/m<sup>3</sup>. The vertical scale is set by  $d_s = 1.00 \text{ pm}$ , and the horizontal scale is set by  $V_s = 20.0 \text{ V}$ . What is the ratio  $C/A$ ?

#### sec. 25-4 Capacitors in Parallel and in Series


- 8 How many  $1.00 \mu\text{F}$  capacitors must be connected in parallel to store a charge of  $1.00 \text{ C}$  with a potential of  $110 \text{ V}$  across the capacitors?

- 9 Each of the uncharged capacitors in Fig. 25-27 has a capacitance of  $25.0 \mu\text{F}$ . A potential difference of  $V = 4200 \text{ V}$  is established when the switch is closed. How many coulombs of charge then pass through meter A?

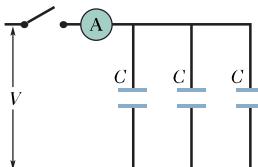


**Fig. 25-27** Problem 9.

- 10 In Fig. 25-28, find the equivalent capacitance of the combination. Assume that  $C_1 = 10.0 \mu\text{F}$ ,  $C_2 = 5.00 \mu\text{F}$ , and  $C_3 = 4.00 \mu\text{F}$ .

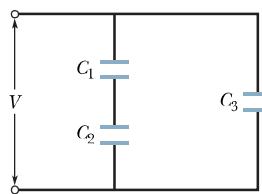

**Fig. 25-28** Problems 10 and 34.


- 11 **ILW** In Fig. 25-29, find the equivalent capacitance of the combination. Assume that  $C_1 = 10.0 \mu\text{F}$ ,  $C_2 = 5.00 \mu\text{F}$ , and  $C_3 = 4.00 \mu\text{F}$ .

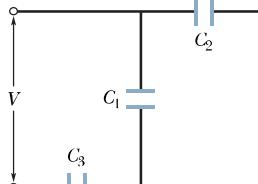

**Fig. 25-29** Problems 11, 17, and 38.

- 12 Two parallel-plate capacitors,  $6.0 \mu\text{F}$  each, are connected in parallel to a  $10 \text{ V}$  battery. One of the capacitors is then squeezed so that its plate separation is  $50.0\%$  of its initial value. Because of the squeezing, (a) how much additional charge is transferred to the capacitors by the battery and (b) what is the increase in the total charge stored on the capacitors?

- 13 **SSM ILW** A  $100 \text{ pF}$  capacitor is charged to a potential difference of  $50 \text{ V}$ , and the charging battery is disconnected. The capacitor is then connected in parallel with a second (initially uncharged) capacitor. If the potential difference across the first capacitor drops to  $35 \text{ V}$ , what is the capacitance of this second capacitor?

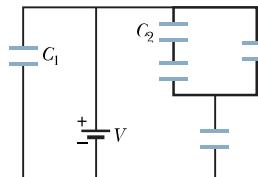


**Fig. 25-30** Problem 14.

- 14 In Fig. 25-30, the battery has a potential difference of  $V = 10.0 \text{ V}$  and the five capacitors each have a capacitance of  $10.0 \mu\text{F}$ . What is the charge on (a) capacitor 1 and (b) capacitor 2?


- 15 **GO** In Fig. 25-31, a  $20.0 \text{ V}$  battery is connected across capacitors of capacitances  $C_1 = C_6 = 3.00 \mu\text{F}$  and  $C_3 = C_5 = 2.00C_2 = 2.00C_4 = 4.00 \mu\text{F}$ . What are (a) the equivalent capacitance  $C_{\text{eq}}$  of the capacitors and (b) the charge stored by  $C_{\text{eq}}$ ? What

are (c)  $V_1$  and (d)  $q_1$  of capacitor 1, (e)  $V_2$  and (f)  $q_2$  of capacitor 2, and (g)  $V_3$  and (h)  $q_3$  of capacitor 3?

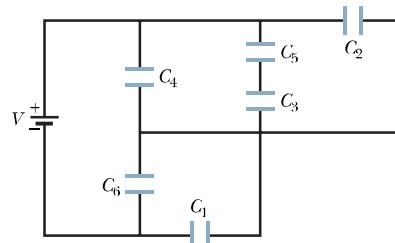

**Fig. 25-31** Problem 15.


- 16 Plot 1 in Fig. 25-32a gives the charge  $q$  that can be stored on capacitor 1 versus the electric potential  $V$  set up across it. The vertical scale is set by  $q_s = 16.0 \mu\text{C}$ , and the horizontal scale is set by  $V_s = 2.0 \text{ V}$ . Plots 2 and 3 are similar plots for capacitors 2 and 3, respectively. Figure 25-32b shows a circuit with those three capacitors and a  $6.0 \text{ V}$  battery. What is the charge stored on capacitor 2 in that circuit?

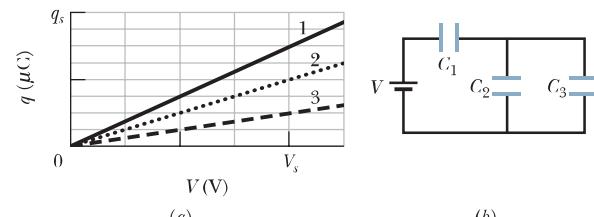

**Fig. 25-32** Problem 16.

- 17 **GO** In Fig. 25-29, a potential difference of  $V = 100.0 \text{ V}$  is applied across a capacitor arrangement with capacitances  $C_1 = 10.0 \mu\text{F}$ ,  $C_2 = 5.00 \mu\text{F}$ , and  $C_3 = 4.00 \mu\text{F}$ . If capacitor 3 undergoes electrical breakdown so that it becomes equivalent to conducting wire, what is the increase in (a) the charge on capacitor 1 and (b) the potential difference across capacitor 1?

- 18 Figure 25-33 shows a circuit section of four air-filled capacitors that is connected to a larger circuit. The graph below the section shows the electric potential  $V(x)$  as a function of position  $x$

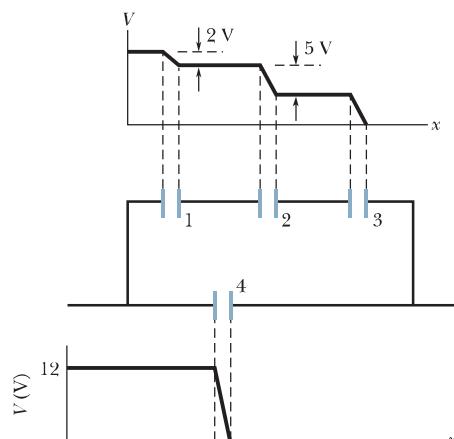

**Fig. 25-33** Problem 18.

along the lower part of the section, through capacitor 4. Similarly, the graph above the section shows the electric potential  $V(x)$  as a function of position  $x$  along the upper part of the section, through capacitors 1, 2, and 3. Capacitor 3 has a capacitance of  $0.80 \mu\text{F}$ . What are the capacitances of (a) capacitor 1 and (b) capacitor 2?

- 19 In Fig. 25-34, the battery has potential difference  $V = 9.0 \text{ V}$ ,  $C_2 = 3.0 \mu\text{F}$ ,  $C_4 = 4.0 \mu\text{F}$ , and all the capacitors are initially uncharged. When switch S is closed, a total charge of  $12 \mu\text{C}$  passes through point a and a total charge of  $8.0 \mu\text{C}$  passes through point b. What are (a)  $C_1$  and (b)  $C_3$ ?

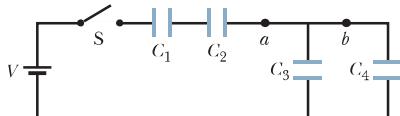


Fig. 25-34 Problem 19.

- 20 Figure 25-35 shows a variable “air gap” capacitor for manual tuning. Alternate plates are connected together; one group of plates is fixed in position, and the other group is capable of rotation. Consider a capacitor of  $n = 8$  plates of alternating polarity, each plate having area  $A = 1.25 \text{ cm}^2$  and separated from adjacent plates by distance  $d = 3.40 \text{ mm}$ . What is the maximum capacitance of the device?

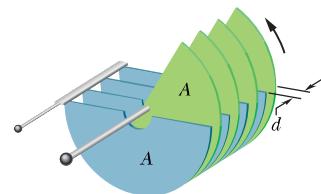


Fig. 25-35 Problem 20.

- 21 SSM WWW In Fig. 25-36, the capacitances are  $C_1 = 1.0 \mu\text{F}$  and  $C_2 = 3.0 \mu\text{F}$ , and both capacitors are charged to a potential difference of  $V = 100 \text{ V}$  but with opposite polarity as shown. Switches  $S_1$  and  $S_2$  are now closed. (a) What is now the potential difference between points a and b? What now is the charge on capacitor (b) 1 and (c) 2?

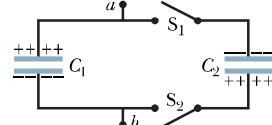


Fig. 25-36 Problem 21.

- 22 In Fig. 25-37,  $V = 10 \text{ V}$ ,  $C_1 = 10 \mu\text{F}$ , and  $C_2 = C_3 = 20 \mu\text{F}$ . Switch S is first thrown to the left side until capacitor 1 reaches equilibrium. Then the switch is thrown to the right. When equilibrium is again reached, how much charge is on capacitor 1?

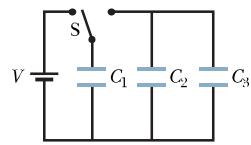


Fig. 25-37 Problem 22.

- 23 The capacitors in Fig. 25-38 are initially uncharged. The capacitances are  $C_1 = 4.0 \mu\text{F}$ ,  $C_2 = 8.0 \mu\text{F}$ , and  $C_3 = 12 \mu\text{F}$ , and the battery's potential difference is  $V = 12 \text{ V}$ . When switch S is closed, how many electrons travel through (a) point a, (b) point b, (c) point c, and (d) point d? In the figure, do the electrons travel up or down through (e) point b and (f) point c?

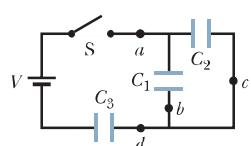


Fig. 25-38 Problem 23.

- 24 Figure 25-39 represents two air-filled cylindrical capacitors connected in series across a battery with potential  $V = 10 \text{ V}$ . Capacitor 1 has an inner plate radius of  $5.0 \text{ mm}$ , an outer plate radius of  $1.5 \text{ cm}$ , and a length of  $5.0 \text{ cm}$ . Capacitor 2 has an inner plate radius

of  $2.5 \text{ mm}$ , an outer plate radius of  $1.0 \text{ cm}$ , and a length of  $9.0 \text{ cm}$ . The outer plate of capacitor 2 is a conducting organic membrane that can be stretched, and the capacitor can be inflated to increase the plate separation. If the outer plate radius is increased to  $2.5 \text{ cm}$  by inflation, (a) how many electrons move through point P and (b) do they move toward or away from the battery?

- 25 In Fig. 25-40, two parallel-plate capacitors (with air between the plates) are connected to a battery. Capacitor 1 has a plate area of  $1.5 \text{ cm}^2$  and an electric field (between its plates) of magnitude  $2000 \text{ V/m}$ . Capacitor 2 has a plate area of  $0.70 \text{ cm}^2$  and an electric field of magnitude  $1500 \text{ V/m}$ . What is the total charge on the two capacitors?

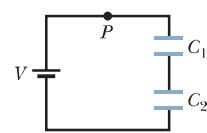


Fig. 25-39 Problem 24.

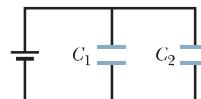


Fig. 25-40 Problem 25.

- 26 Capacitor 3 in Fig. 25-41a is a *variable capacitor* (its capacitance  $C_3$  can be varied). Figure 25-41b gives the electric potential  $V_1$  across capacitor 1 versus  $C_3$ . The horizontal scale is set by  $C_{3s} = 12.0 \mu\text{F}$ . Electric potential  $V_1$  approaches an asymptote of  $10 \text{ V}$  as  $C_3 \rightarrow \infty$ . What are (a) the electric potential  $V$  across the battery, (b)  $C_1$ , and (c)  $C_2$ ?

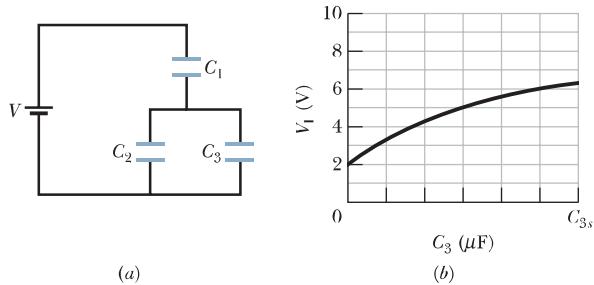


Fig. 25-41 Problem 26.

- 27 Figure 25-42 shows a  $12.0 \text{ V}$  battery and four uncharged capacitors of capacitances  $C_1 = 1.00 \mu\text{F}$ ,  $C_2 = 2.00 \mu\text{F}$ ,  $C_3 = 3.00 \mu\text{F}$ , and  $C_4 = 4.00 \mu\text{F}$ . If only switch  $S_1$  is closed, what is the charge on (a) capacitor 1, (b) capacitor 2, (c) capacitor 3, and (d) capacitor 4? If both switches are closed, what is the charge on (e) capacitor 1, (f) capacitor 2, (g) capacitor 3, and (h) capacitor 4?

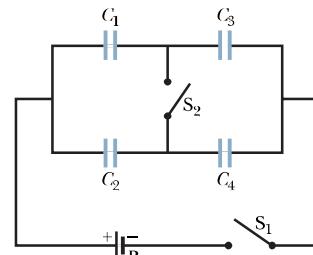


Fig. 25-42 Problem 27.

- 28 Figure 25-43 displays a  $12.0 \text{ V}$  battery and 3 uncharged capacitors of capacitances  $C_1 = 4.00 \mu\text{F}$ ,  $C_2 = 6.00 \mu\text{F}$ , and  $C_3 = 3.00 \mu\text{F}$ . The switch is thrown to the left side until capacitor 1 is fully charged. Then the switch is thrown to the right. What is the final charge on (a) capacitor 1, (b) capacitor 2, and (c) capacitor 3?

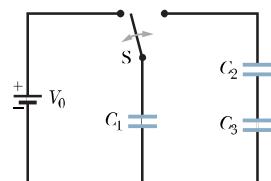


Fig. 25-43 Problem 28.

**sec. 25-5 Energy Stored in an Electric Field**

**•29** What capacitance is required to store an energy of  $10 \text{ kW} \cdot \text{h}$  at a potential difference of  $1000 \text{ V}$ ?

**•30** How much energy is stored in  $1.00 \text{ m}^3$  of air due to the “fair weather” electric field of magnitude  $150 \text{ V/m}$ ?

**•31 SSM** A  $2.0 \mu\text{F}$  capacitor and a  $4.0 \mu\text{F}$  capacitor are connected in parallel across a  $300 \text{ V}$  potential difference. Calculate the total energy stored in the capacitors.

**•32** A parallel-plate air-filled capacitor having area  $40 \text{ cm}^2$  and plate spacing  $1.0 \text{ mm}$  is charged to a potential difference of  $600 \text{ V}$ . Find (a) the capacitance, (b) the magnitude of the charge on each plate, (c) the stored energy, (d) the electric field between the plates, and (e) the energy density between the plates.

**•33** A charged isolated metal sphere of diameter  $10 \text{ cm}$  has a potential of  $8000 \text{ V}$  relative to  $V = 0$  at infinity. Calculate the energy density in the electric field near the surface of the sphere.

**•34** In Fig. 25-28, a potential difference  $V = 100 \text{ V}$  is applied across a capacitor arrangement with capacitances  $C_1 = 10.0 \mu\text{F}$ ,  $C_2 = 5.00 \mu\text{F}$ , and  $C_3 = 4.00 \mu\text{F}$ . What are (a) charge  $q_3$ , (b) potential difference  $V_3$ , and (c) stored energy  $U_3$  for capacitor 3, (d)  $q_1$ , (e)  $V_1$ , and (f)  $U_1$  for capacitor 1, and (g)  $q_2$ , (h)  $V_2$ , and (i)  $U_2$  for capacitor 2?

**•35** Assume that a stationary electron is a point of charge. What is the energy density  $u$  of its electric field at radial distances (a)  $r = 1.00 \text{ mm}$ , (b)  $r = 1.00 \mu\text{m}$ , (c)  $r = 1.00 \text{ nm}$ , and (d)  $r = 1.00 \text{ pm}$ ? (e) What is  $u$  in the limit as  $r \rightarrow 0$ ?


**•36** As a safety engineer, you must evaluate the practice of storing flammable conducting liquids in nonconducting containers. The company supplying a certain liquid has been using a squat, cylindrical plastic container of radius  $r = 0.20 \text{ m}$  and filling it to height  $h = 10 \text{ cm}$ , which is not the container’s full interior height (Fig. 25-44). Your investigation reveals that during handling at the company, the exterior surface of the container commonly acquires a negative charge density of magnitude  $2.0 \mu\text{C/m}^2$  (approximately uniform). Because the liquid is a conducting material, the charge on the container induces charge separation within the liquid. (a) How much negative charge is induced in the center of the liquid’s bulk? (b) Assume the capacitance of the central portion of the liquid relative to ground is  $35 \text{ pF}$ . What is the potential energy associated with the negative charge in that effective capacitor? (c) If a spark occurs between the ground and the central portion of the liquid (through the venting port), the potential energy can be fed into the spark. The minimum spark energy needed to ignite the liquid is  $10 \text{ mJ}$ . In this situation, can a spark ignite the liquid?

**•37 SSM ILW WWW** The parallel plates in a capacitor, with a plate area of  $8.50 \text{ cm}^2$  and an air-filled separation of  $3.00 \text{ mm}$ , are charged by a  $6.00 \text{ V}$  battery. They are then disconnected from the battery and pulled apart (without discharge) to a separation of  $8.00 \text{ mm}$ . Neglecting fringing, find (a) the potential difference between the plates, (b) the initial stored energy, (c) the final stored energy, and (d) the work required to separate the plates.

**•38** In Fig. 25-29, a potential difference  $V = 100 \text{ V}$  is applied across a capacitor arrangement with capacitances  $C_1 = 10.0 \mu\text{F}$ ,

$C_2 = 5.00 \mu\text{F}$ , and  $C_3 = 15.0 \mu\text{F}$ . What are (a) charge  $q_3$ , (b) potential difference  $V_3$ , and (c) stored energy  $U_3$  for capacitor 3, (d)  $q_1$ , (e)  $V_1$ , and (f)  $U_1$  for capacitor 1, and (g)  $q_2$ , (h)  $V_2$ , and (i)  $U_2$  for capacitor 2?

**•39** In Fig. 25-45,  $C_1 = 10.0 \mu\text{F}$ ,  $C_2 = 20.0 \mu\text{F}$ , and  $C_3 = 25.0 \mu\text{F}$ . If no capacitor can withstand a potential difference of more than  $100 \text{ V}$  without failure, what are (a) the magnitude of the maximum potential difference that can exist between points  $A$  and  $B$  and (b) the maximum energy that can be stored in the three-capacitor arrangement?

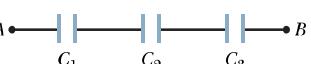

**Fig. 25-45** Problem 39.

**sec. 25-6 Capacitor with a Dielectric**

**•40** An air-filled parallel-plate capacitor has a capacitance of  $1.3 \text{ pF}$ . The separation of the plates is doubled, and wax is inserted between them. The new capacitance is  $2.6 \text{ pF}$ . Find the dielectric constant of the wax.

**•41 SSM** A coaxial cable used in a transmission line has an inner radius of  $0.10 \text{ mm}$  and an outer radius of  $0.60 \text{ mm}$ . Calculate the capacitance per meter for the cable. Assume that the space between the conductors is filled with polystyrene.


**•42** A parallel-plate air-filled capacitor has a capacitance of  $50 \text{ pF}$ . (a) If each of its plates has an area of  $0.35 \text{ m}^2$ , what is the separation? (b) If the region between the plates is now filled with material having  $\kappa = 5.6$ , what is the capacitance?

**•43** Given a  $7.4 \text{ pF}$  air-filled capacitor, you are asked to convert it to a capacitor that can store up to  $7.4 \mu\text{J}$  with a maximum potential difference of  $652 \text{ V}$ . Which dielectric in Table 25-1 should you use to fill the gap in the capacitor if you do not allow for a margin of error?

**•44** You are asked to construct a capacitor having a capacitance near  $1 \text{ nF}$  and a breakdown potential in excess of  $10\,000 \text{ V}$ . You think of using the sides of a tall Pyrex drinking glass as a dielectric, lining the inside and outside curved surfaces with aluminum foil to act as the plates. The glass is  $15 \text{ cm}$  tall with an inner radius of  $3.6 \text{ cm}$  and an outer radius of  $3.8 \text{ cm}$ . What are the (a) capacitance and (b) breakdown potential of this capacitor?

**•45** A certain parallel-plate capacitor is filled with a dielectric for which  $\kappa = 5.5$ . The area of each plate is  $0.034 \text{ m}^2$ , and the plates are separated by  $2.0 \text{ mm}$ . The capacitor will fail (short out and burn up) if the electric field between the plates exceeds  $200 \text{ kN/C}$ . What is the maximum energy that can be stored in the capacitor?

**•46** In Fig. 25-46, how much charge is stored on the parallel-plate capacitors by the  $12.0 \text{ V}$  battery? One is filled with air, and the other is filled with a dielectric for which  $\kappa = 3.00$ ; both capacitors have a plate area of  $5.00 \times 10^{-3} \text{ m}^2$  and a plate separation of  $2.00 \text{ mm}$ .

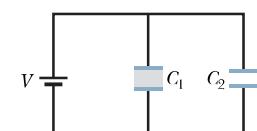

**Fig. 25-46** Problem 46.

**•47 SSM ILW** A certain substance has a dielectric constant of 2.8 and a dielectric strength of  $18 \text{ MV/m}$ . If it is used as the dielectric material in a parallel-plate capacitor, what minimum area should the plates of the capacitor have to obtain a capacitance of  $7.0 \times 10^{-2} \mu\text{F}$  and to ensure that the capacitor will be able to withstand a potential difference of  $4.0 \text{ kV}$ ?

- 48** Figure 25-47 shows a parallel-plate capacitor with a plate area  $A = 5.56 \text{ cm}^2$  and separation  $d = 5.56 \text{ mm}$ . The left half of the gap is filled with material of dielectric constant  $\kappa_1 = 7.00$ ; the right half is filled with material of dielectric constant  $\kappa_2 = 12.0$ . What is the capacitance?

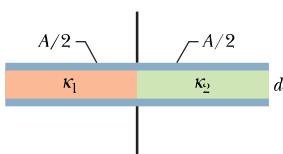


Fig. 25-47 Problem 48.

- 49** Figure 25-48 shows a parallel-plate capacitor with a plate area  $A = 7.89 \text{ cm}^2$  and plate separation  $d = 4.62 \text{ mm}$ . The top half of the gap is filled with material of dielectric constant  $\kappa_1 = 11.0$ ; the bottom half is filled with material of dielectric constant  $\kappa_2 = 12.0$ . What is the capacitance?

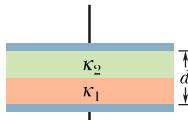


Fig. 25-48 Problem 49.

- 50** Figure 25-49 shows a parallel-plate capacitor of plate area  $A = 10.5 \text{ cm}^2$  and plate separation  $2d = 7.12 \text{ mm}$ . The left half of the gap is filled with material of dielectric constant  $\kappa_1 = 21.0$ ; the top of the right half is filled with material of dielectric constant  $\kappa_2 = 42.0$ ; the bottom of the right half is filled with material of dielectric constant  $\kappa_3 = 58.0$ . What is the capacitance?

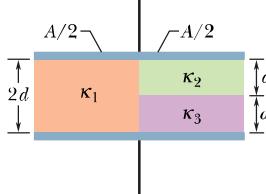


Fig. 25-49 Problem 50.

### sec. 25-8 Dielectrics and Gauss' Law

- 51 SSM WWW** A parallel-plate capacitor has a capacitance of 100 pF, a plate area of  $100 \text{ cm}^2$ , and a mica dielectric ( $\kappa = 5.4$ ) completely filling the space between the plates. At 50 V potential difference, calculate (a) the electric field magnitude  $E$  in the mica, (b) the magnitude of the free charge on the plates, and (c) the magnitude of the induced surface charge on the mica.

- 52** For the arrangement of Fig. 25-17, suppose that the battery remains connected while the dielectric slab is being introduced. Calculate (a) the capacitance, (b) the charge on the capacitor plates, (c) the electric field in the gap, and (d) the electric field in the slab, after the slab is in place.

- 53** A parallel-plate capacitor has plates of area  $0.12 \text{ m}^2$  and a separation of 1.2 cm. A battery charges the plates to a potential difference of 120 V and is then disconnected. A dielectric slab of thickness 4.0 mm and dielectric constant 4.8 is then placed symmetrically between the plates. (a) What is the capacitance before the slab is inserted? (b) What is the capacitance with the slab in place? What is the free charge  $q$  (c) before and (d) after the slab is inserted? What is the magnitude of the electric field (e) in the space between the plates and dielectric and (f) in the dielectric itself? (g) With the slab in place, what is the potential difference across the plates? (h) How much external work is involved in inserting the slab?

- 54** Two parallel plates of area  $100 \text{ cm}^2$  are given charges of equal magnitudes  $8.9 \times 10^{-7} \text{ C}$  but opposite signs. The electric field within the dielectric material filling the space between the plates is  $1.4 \times 10^6 \text{ V/m}$ . (a) Calculate the dielectric constant of the material. (b) Determine the magnitude of the charge induced on each dielectric surface.

- 55** The space between two concentric conducting spherical shells of radii  $b = 1.70 \text{ cm}$  and  $a = 1.20 \text{ cm}$  is filled with a sub-

stance of dielectric constant  $\kappa = 23.5$ . A potential difference  $V = 73.0 \text{ V}$  is applied across the inner and outer shells. Determine (a) the capacitance of the device, (b) the free charge  $q$  on the inner shell, and (c) the charge  $q'$  induced along the surface of the inner shell.

### Additional Problems

- 56** In Fig. 25-50, the battery potential difference  $V$  is 10.0 V and each of the seven capacitors has capacitance  $10.0 \mu\text{F}$ . What is the charge on (a) capacitor 1 and (b) capacitor 2?

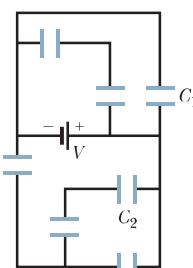


Fig. 25-50 Problem 56.

- 57 SSM** In Fig. 25-51,  $V = 9.0 \text{ V}$ ,  $C_1 = C_2 = 30 \mu\text{F}$ , and  $C_3 = C_4 = 15 \mu\text{F}$ . What is the charge on capacitor 4?

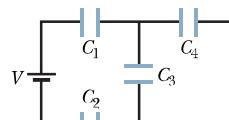


Fig. 25-51 Problem 57.

- 58** The capacitances of the four capacitors shown in Fig. 25-52 are given in terms of a certain quantity  $C$ . (a) If  $C = 50 \mu\text{F}$ , what is the equivalent capacitance between points  $A$  and  $B$ ? (Hint:

First imagine that a battery is connected between those two points; then reduce the circuit to an equivalent capacitance.) (b) Repeat for points  $A$  and  $D$ .

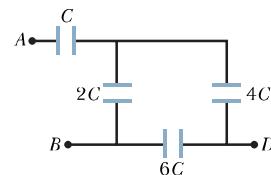


Fig. 25-52 Problem 58.

- 59** In Fig. 25-53,  $V = 12 \text{ V}$ ,  $C_1 = C_4 = 2.0 \mu\text{F}$ ,  $C_2 = 4.0 \mu\text{F}$ , and  $C_3 = 1.0 \mu\text{F}$ . What is the charge on capacitor 4?

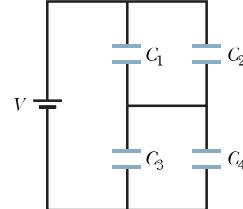


Fig. 25-53 Problem 59.

- 60** *The chocolate crumb mystery.* This story begins with Problem 60 in Chapter 23. As part of the investigation of the biscuit factory explosion, the electric potentials of the workers were measured as they emptied sacks of chocolate crumb powder into the loading bin, stirring up a cloud of the powder around themselves. Each worker had an electric potential of about 7.0 kV relative to the ground, which was taken as zero potential. (a) Assuming that each worker was effectively a capacitor with a typical capacitance of 200 pF, find the energy stored in that effective capacitor. If a single spark between the worker and any conducting object connected to the ground neutralized the worker, that energy would be transferred to the spark. According to measurements, a spark that could ignite a cloud of chocolate crumb powder, and thus set off an explosion, had to have an energy of at least 150 mJ. (b) Could a spark from a worker have set off an explosion in the cloud of powder in the loading bin? (The story continues with Problem 60 in Chapter 26.)

- 61** Figure 25-54 shows capacitor 1 ( $C_1 = 8.00 \mu\text{F}$ ), capacitor 2 ( $C_2 = 6.00 \mu\text{F}$ ), and capacitor 3 ( $C_3 = 8.00 \mu\text{F}$ ) connected to a 12.0 V battery. When switch S is closed so as to connect uncharged ca-

## PROBLEMS

681

pacitor 4 ( $C_4 = 6.00 \mu\text{F}$ ), (a) how much charge passes through point  $P$  from the battery and (b) how much charge shows up on capacitor 4? (c) Explain the discrepancy in those two results.

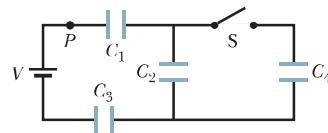


Fig. 25-54 Problem 61.

**62** Two air-filled, parallel-plate capacitors are to be connected to a 10 V battery, first individually, then in series, and then in parallel. In those arrangements, the energy stored in the capacitors turns out to be, listed least to greatest:  $75 \mu\text{J}$ ,  $100 \mu\text{J}$ ,  $300 \mu\text{J}$ , and  $400 \mu\text{J}$ . Of the two capacitors, what is the (a) smaller and (b) greater capacitance?

**63** Two parallel-plate capacitors,  $6.0 \mu\text{F}$  each, are connected in series to a 10 V battery. One of the capacitors is then squeezed so that its plate separation is halved. Because of the squeezing, (a) how much additional charge is transferred to the capacitors by the battery and (b) what is the increase in the *total* charge stored on the capacitors (the charge on the positive plate of one capacitor plus the charge on the positive plate of the other capacitor)?

**64** In Fig. 25-55,  $V = 12 \text{ V}$ ,  $C_1 = C_5 = C_6 = 6.0 \mu\text{F}$ , and  $C_2 = C_3 = C_4 = 4.0 \mu\text{F}$ . What are (a) the net charge stored on the capacitors and (b) the charge on capacitor 4?

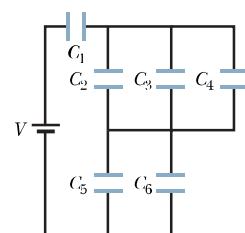
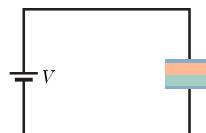


Fig. 25-55 Problem 64.

**65 SSM** In Fig. 25-56, the parallel-plate capacitor of plate area  $2.00 \times 10^{-2} \text{ m}^2$  is filled with two dielectric slabs, each with thickness 2.00 mm. One slab has dielectric constant 3.00, and the other, 4.00. How much charge does the 7.00 V battery store on the capacitor?

Fig. 25-56  
Problem 65.

**66** A cylindrical capacitor has radii  $a$  and  $b$  as in Fig. 25-6. Show that half the stored electric potential energy lies within a cylinder whose radius is  $r = \sqrt{ab}$ .

**67** A capacitor of capacitance  $C_1 = 6.00 \mu\text{F}$  is connected in series with a capacitor of capacitance  $C_2 = 4.00 \mu\text{F}$ , and a potential difference of 200 V is applied across the pair. (a) Calculate the equivalent capacitance. What are (b) charge  $q_1$  and (c) potential difference  $V_1$  on capacitor 1 and (d)  $q_2$  and (e)  $V_2$  on capacitor 2?

**68** Repeat Problem 67 for the same two capacitors but with them now connected in parallel.

**69** A certain capacitor is charged to a potential difference  $V$ . If you wish to increase its stored energy by 10%, by what percentage should you increase  $V$ ?

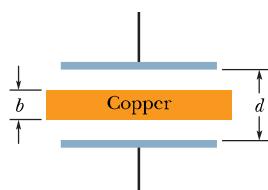


Fig. 25-57 Problems 70 and 71.

**70** A slab of copper of thickness  $b = 2.00 \text{ mm}$  is thrust into a parallel-plate capacitor of plate area  $A = 2.40 \text{ cm}^2$  and plate separation  $d = 5.00 \text{ mm}$ , as shown in Fig. 25-57; the

slab is exactly halfway between the plates. (a) What is the capacitance after the slab is introduced? (b) If a charge  $q = 3.40 \mu\text{C}$  is maintained on the plates, what is the ratio of the stored energy before to that after the slab is inserted? (c) How much work is done on the slab as it is inserted? (d) Is the slab sucked in or must it be pushed in?

**71** Repeat Problem 70, assuming that a potential difference  $V = 85.0 \text{ V}$ , rather than the charge, is held constant.

**72** A potential difference of 300 V is applied to a series connection of two capacitors of capacitances  $C_1 = 2.00 \mu\text{F}$  and  $C_2 = 8.00 \mu\text{F}$ . What are (a) charge  $q_1$  and (b) potential difference  $V_1$  on capacitor 1 and (c)  $q_2$  and (d)  $V_2$  on capacitor 2? The charged capacitors are then disconnected from each other and from the battery. Then the capacitors are reconnected with plates of the *same* signs wired together (the battery is not used). What now are (e)  $q_1$ , (f)  $V_1$ , (g)  $q_2$ , and (h)  $V_2$ ? Suppose, instead, the capacitors charged in part (a) are reconnected with plates of *opposite* signs wired together. What now are (i)  $q_1$ , (j)  $V_1$ , (k)  $q_2$ , and (l)  $V_2$ ?

**73** Figure 25-58 shows a four-capacitor arrangement that is connected to a larger circuit at points  $A$  and  $B$ . The capacitances are  $C_1 = 10 \mu\text{F}$  and  $C_2 = C_3 = C_4 = 20 \mu\text{F}$ . The charge on capacitor 1 is  $30 \mu\text{C}$ . What is the magnitude of the potential difference  $V_A - V_B$ ?

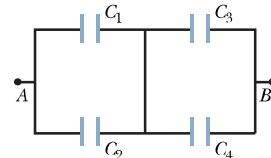


Fig. 25-58 Problem 73.

**74** You have two plates of copper, a sheet of mica (thickness = 0.10 mm,  $\kappa = 5.4$ ), a sheet of glass (thickness = 2.0 mm,  $\kappa = 7.0$ ), and a slab of paraffin (thickness = 1.0 cm,  $\kappa = 2.0$ ). To make a parallel-plate capacitor with the largest  $C$ , which sheet should you place between the copper plates?

**75** A capacitor of unknown capacitance  $C$  is charged to 100 V and connected across an initially uncharged  $60 \mu\text{F}$  capacitor. If the final potential difference across the  $60 \mu\text{F}$  capacitor is 40 V, what is  $C$ ?

**76** A 10 V battery is connected to a series of  $n$  capacitors, each of capacitance  $2.0 \mu\text{F}$ . If the total stored energy is  $25 \mu\text{J}$ , what is  $n$ ?

**77 SSM** In Fig. 25-59, two parallel-plate capacitors  $A$  and  $B$  are connected in parallel across a 600 V battery. Each plate has area  $80.0 \text{ cm}^2$ ; the plate separations are 3.00 mm. Capacitor  $A$  is filled with air; capacitor  $B$  is filled with a dielectric of dielectric constant  $\kappa = 2.60$ . Find the magnitude of the electric field within (a) the dielectric of capacitor  $B$  and (b) the air of capacitor  $A$ . What are the free charge densities  $\sigma$  on the higher-potential plate of (c) capacitor  $A$  and (d) capacitor  $B$ ? (e) What is the induced charge density  $\sigma'$  on the top surface of the dielectric?

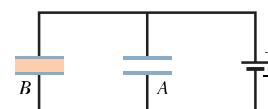


Fig. 25-59 Problem 77.

**78** You have many  $2.0 \mu\text{F}$  capacitors, each capable of withstanding 200 V without undergoing electrical breakdown (in which they conduct charge instead of storing it). How would you assemble a combination having an equivalent capacitance of (a)  $0.40 \mu\text{F}$  and (b)  $1.2 \mu\text{F}$ , each combination capable of withstanding 1000 V?